


Designing a calculator FSM

<https://www.theonlinecalculator.com/>

PLEASE PLEASE PLEASE
NAME YOUR STATES
MEANINGFULLY


Consider a 4-function calculator

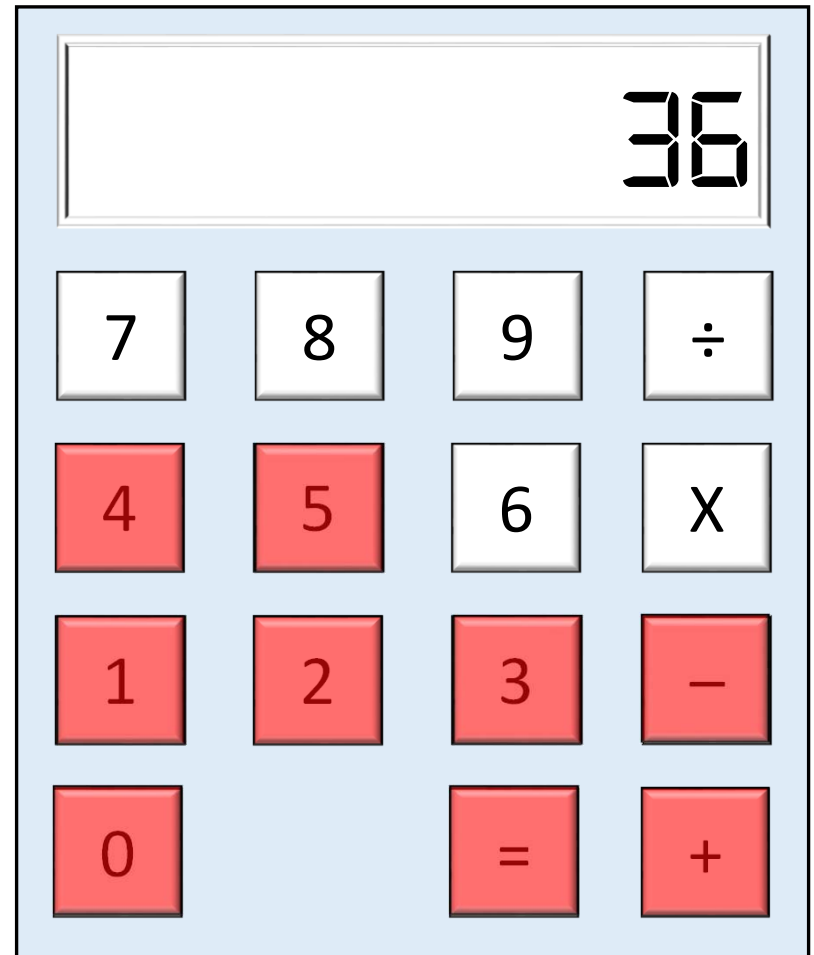
How does the calculator know what to display?





Design the FSM for parsing an input string for a calculator

What must the finite state machine remember to execute the operation

$1+2?$ 


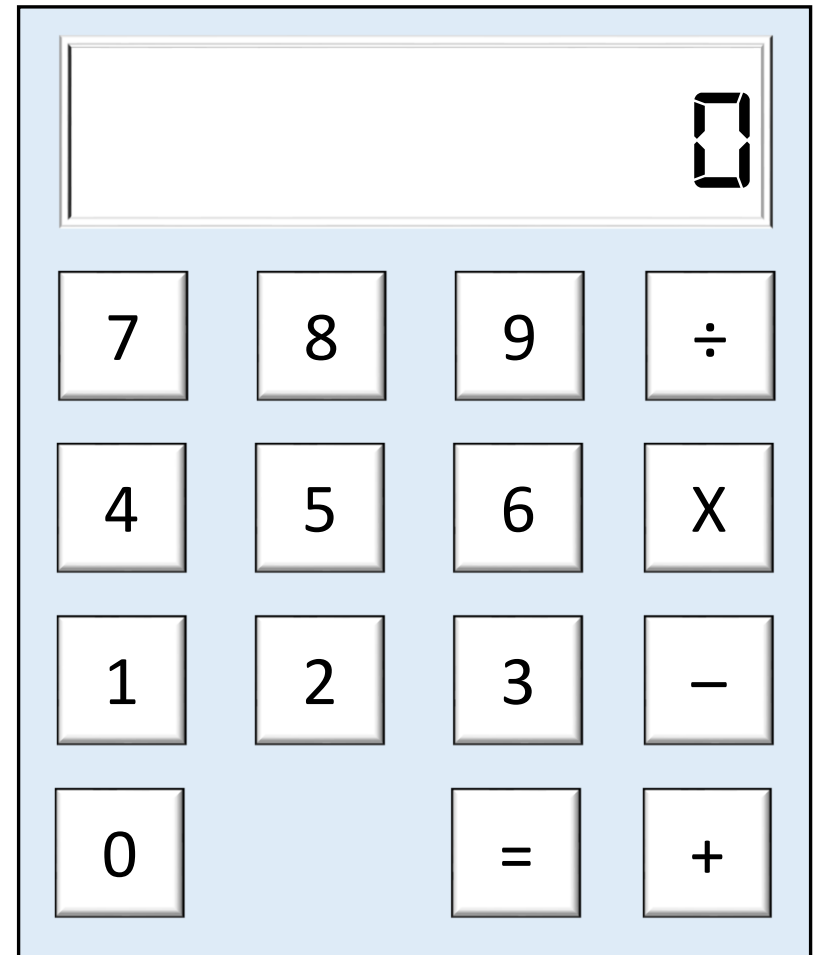


Remember the first operand

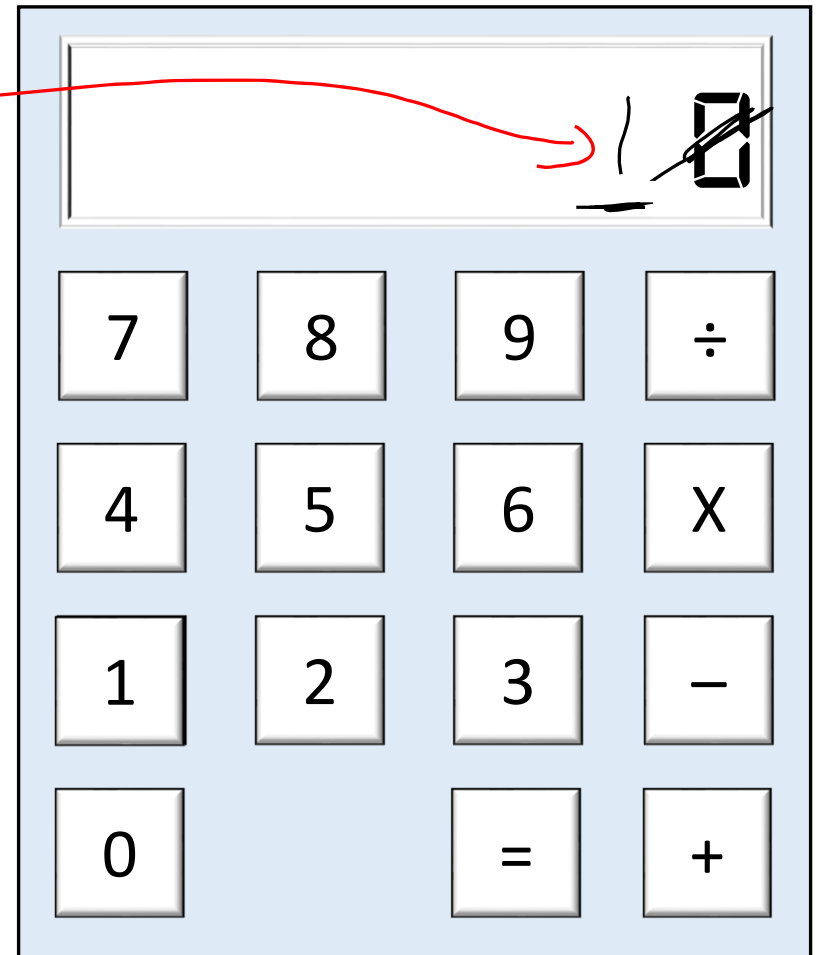
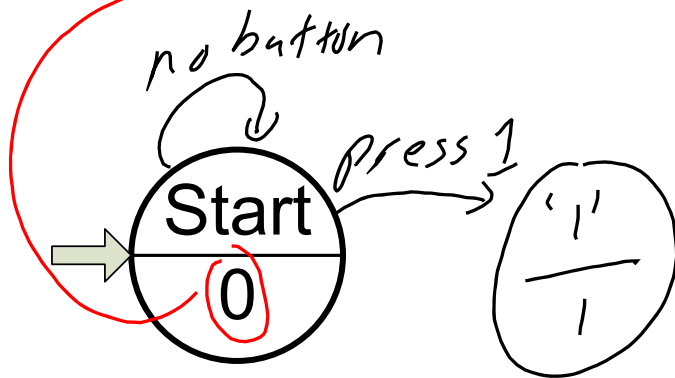


a) No new state b) new state

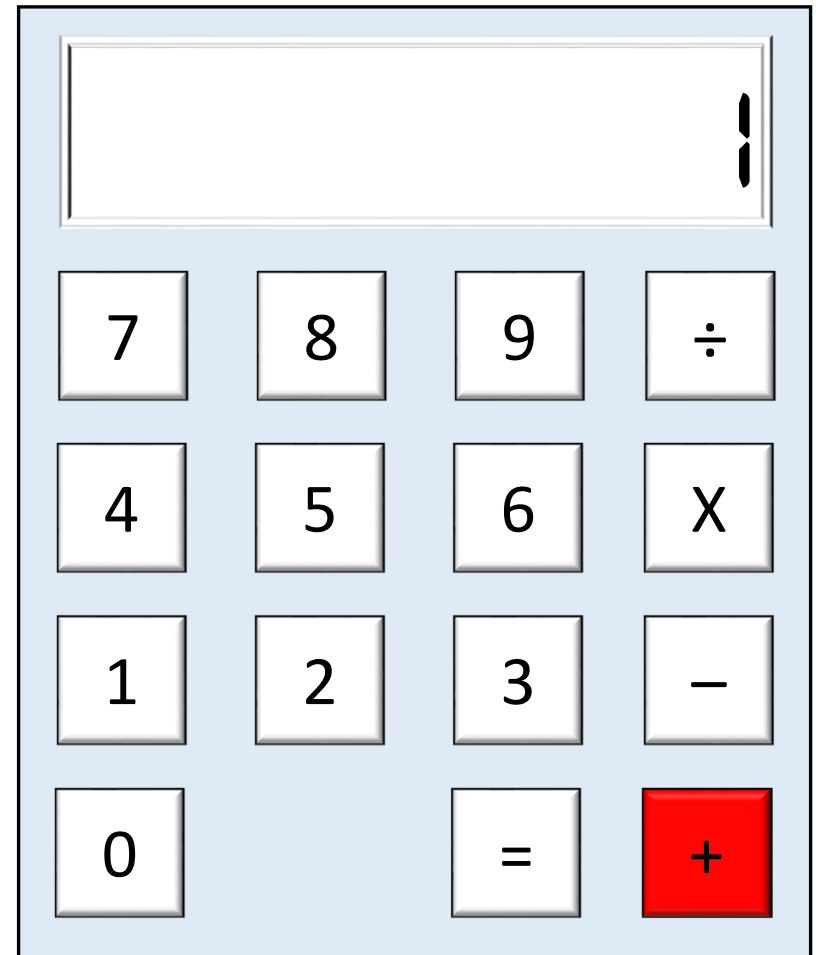
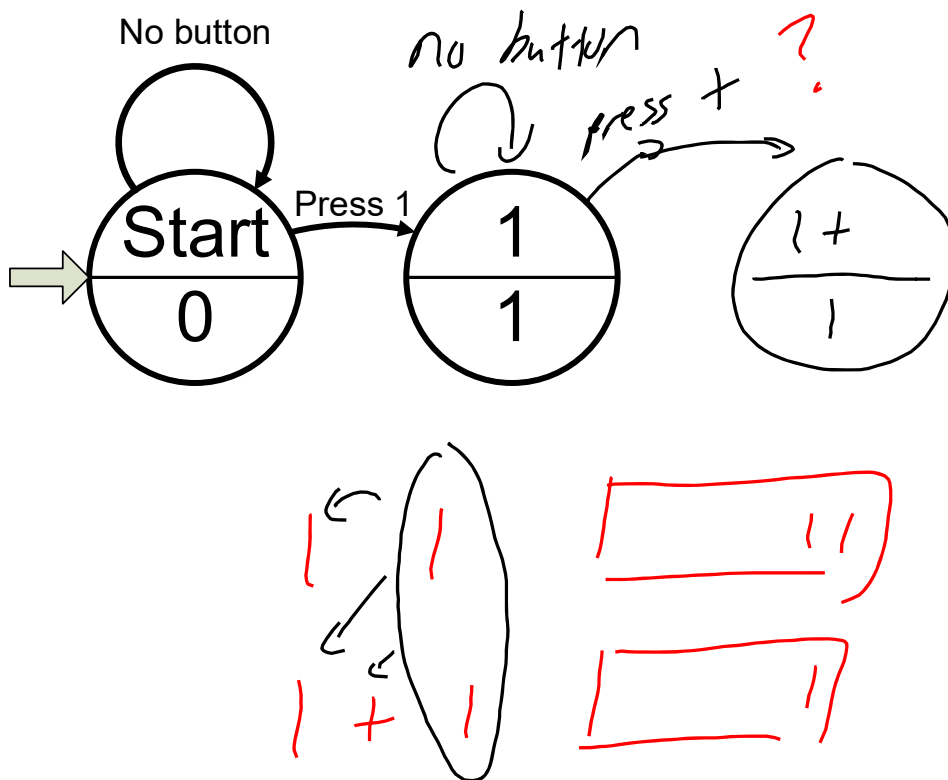
A) No new state B) New state
Remember the operator





Remember the second operand

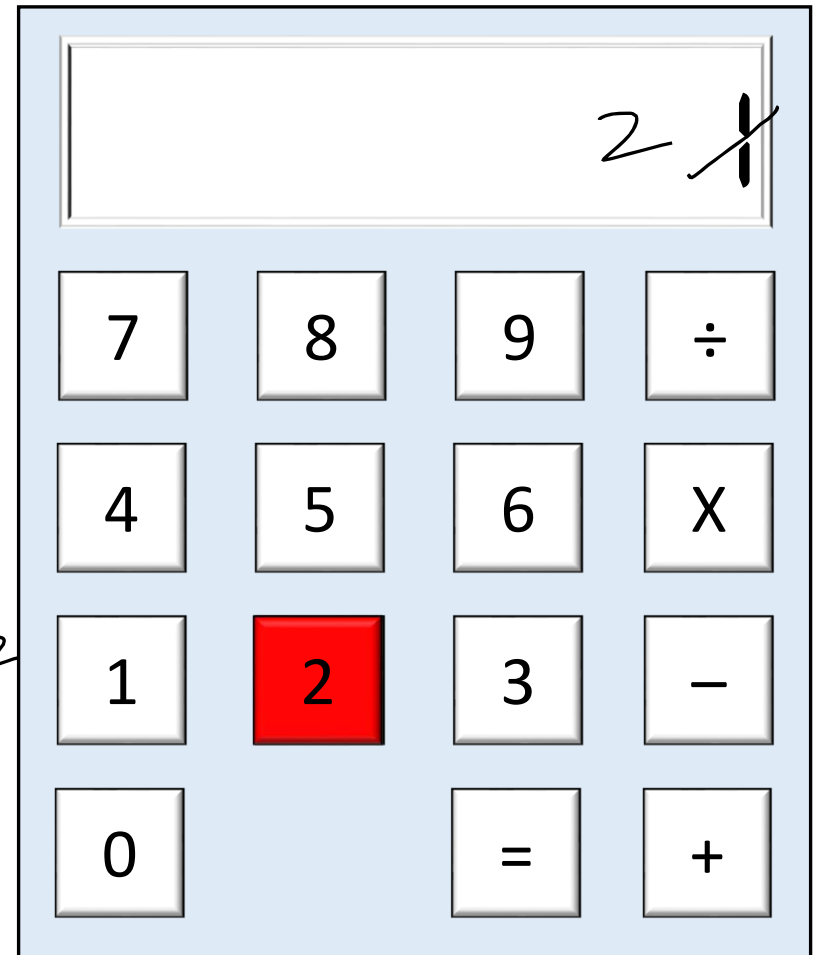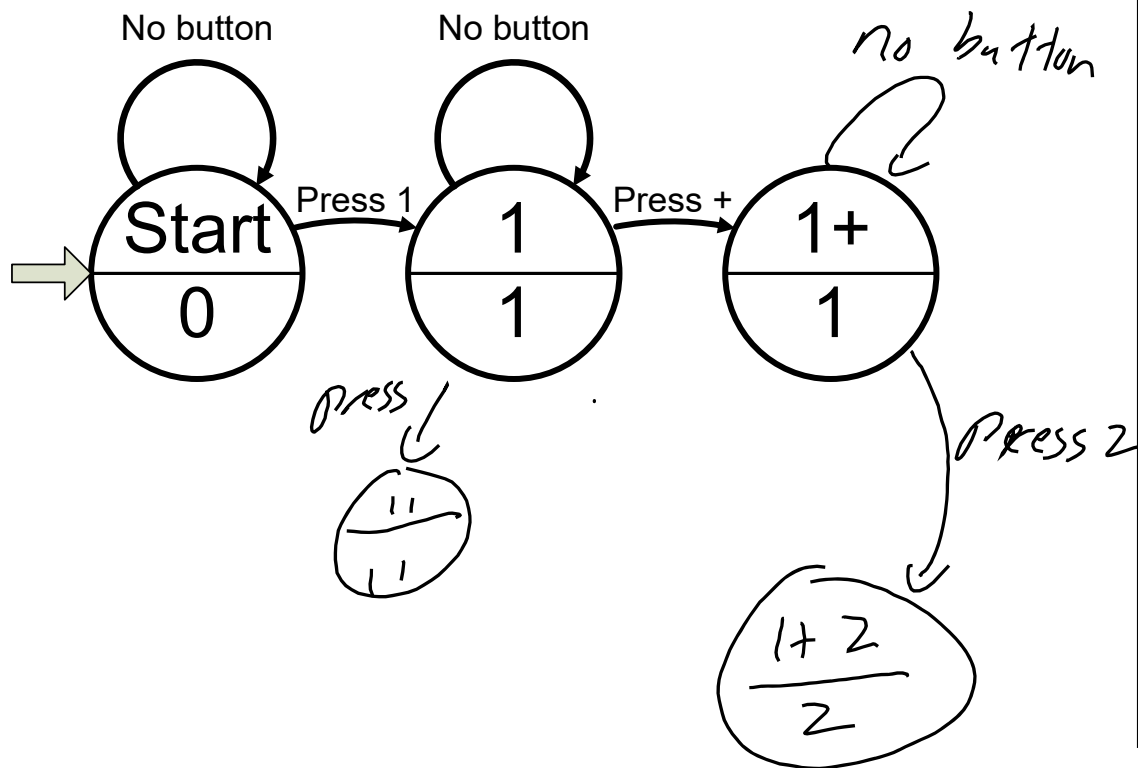


Remember the result

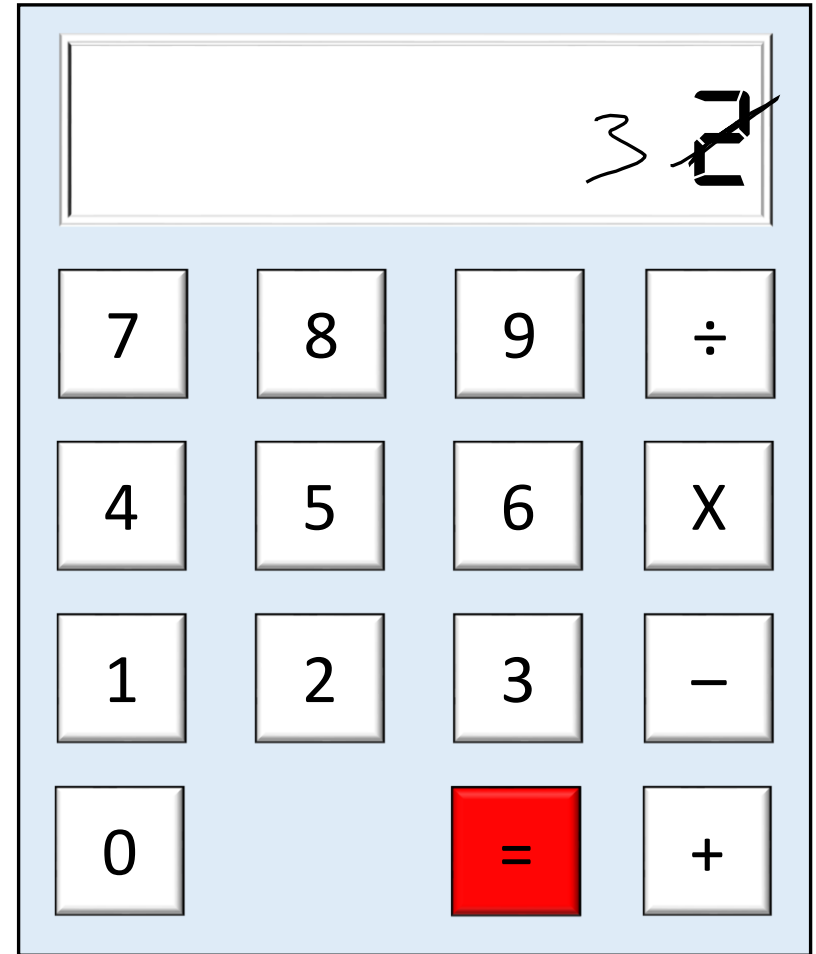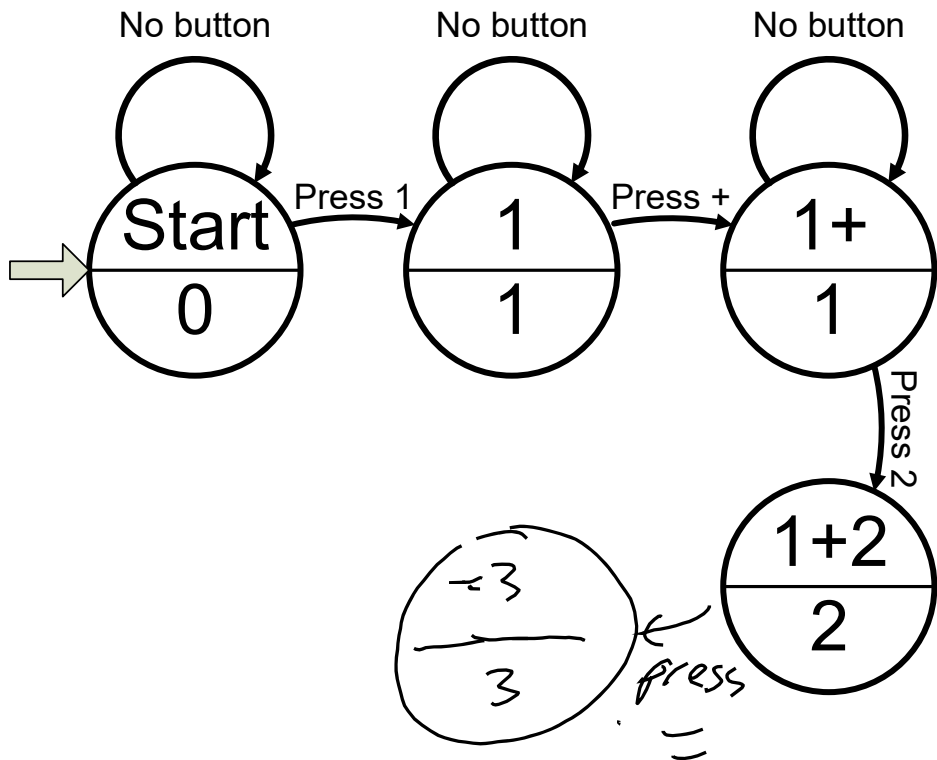

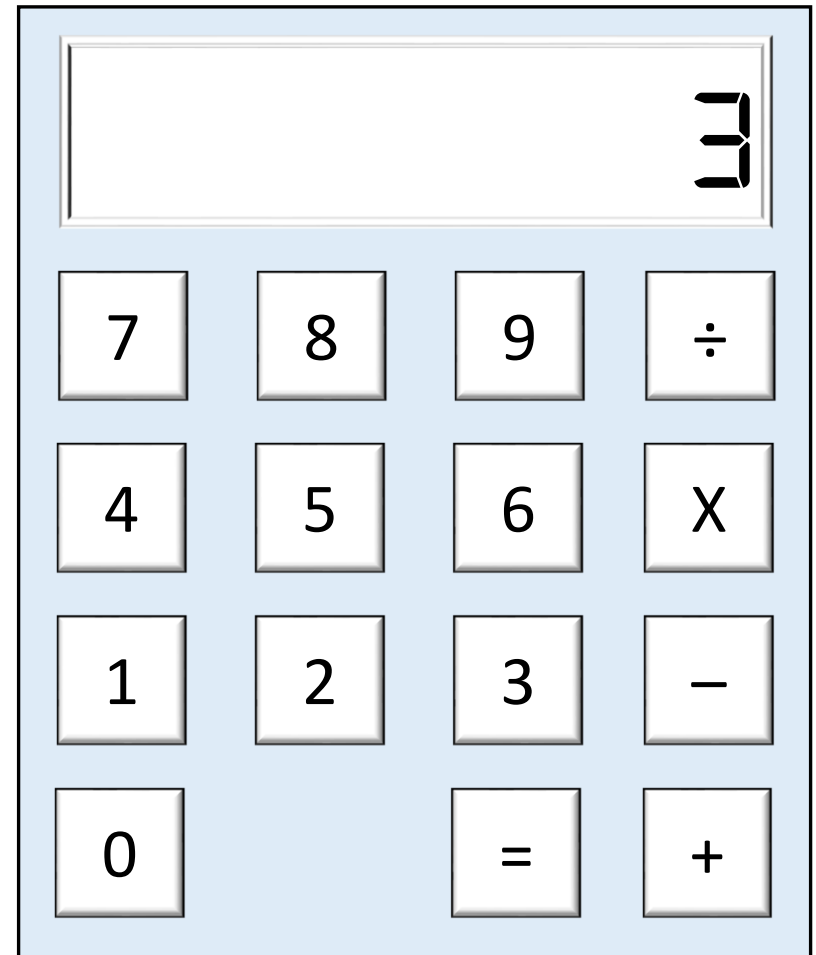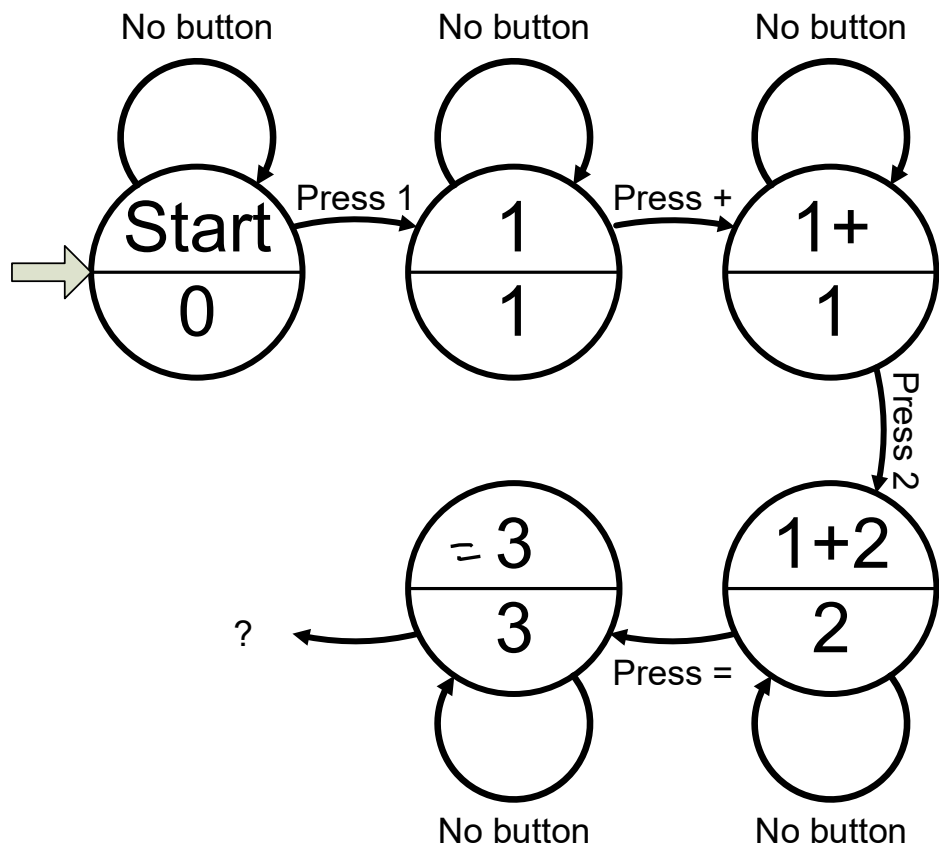
Our first attempt at a FSM for the calculator



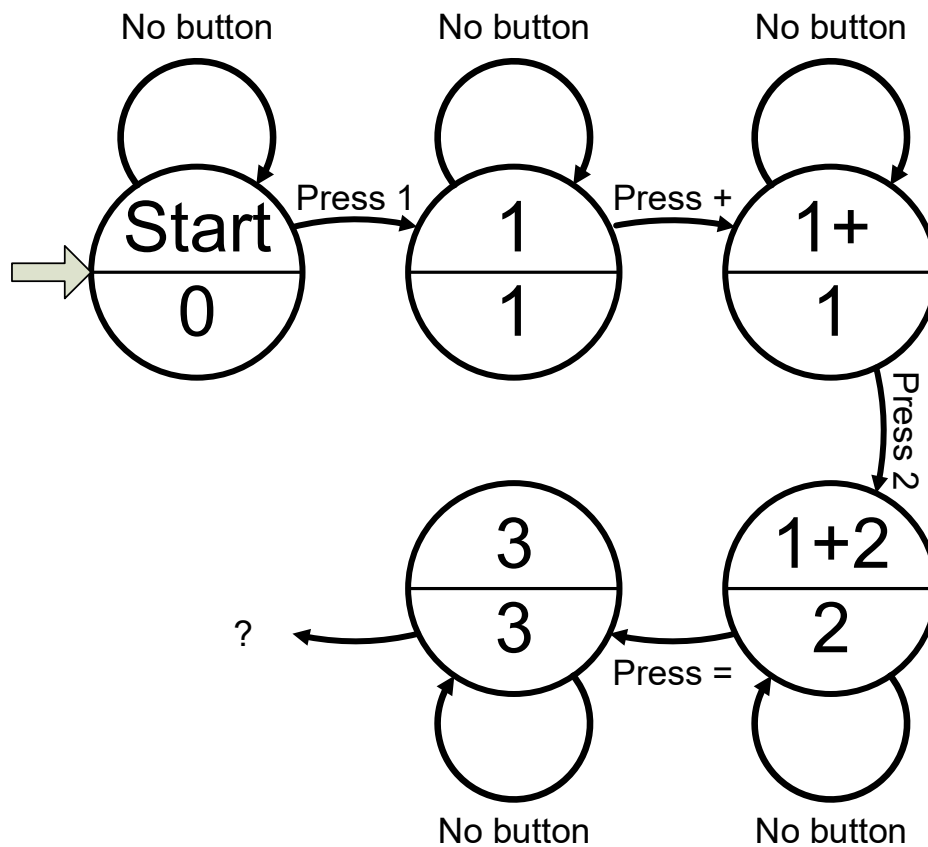What must the FSM remember to execute the operation 1+2?



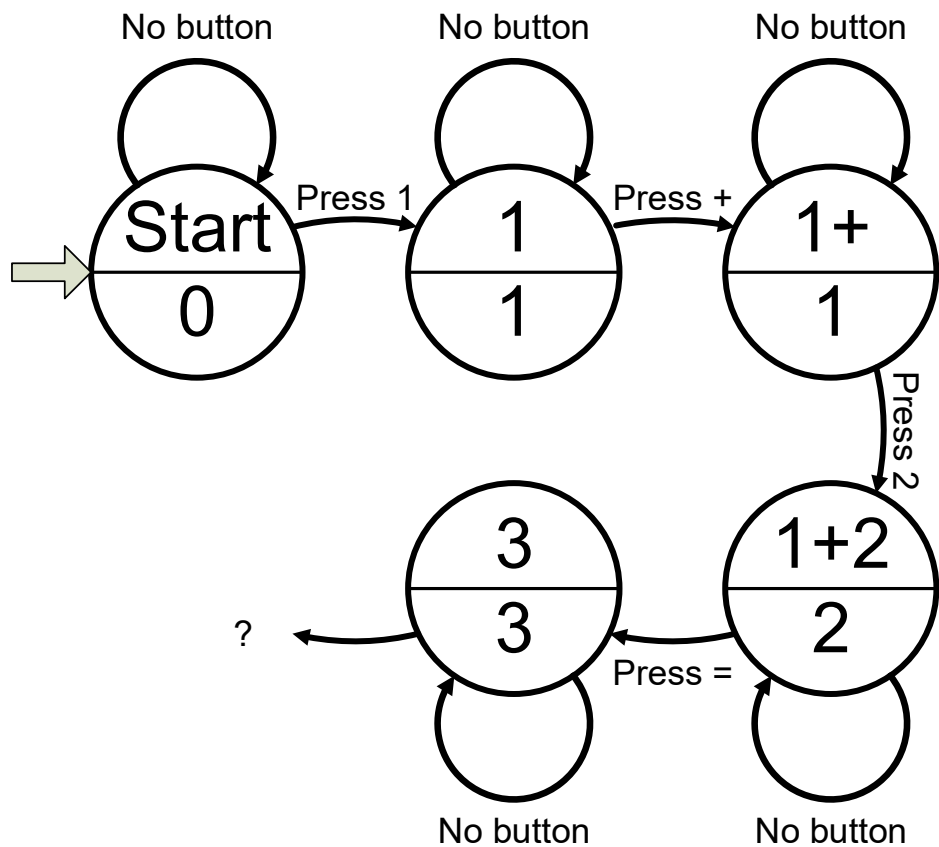
What must the FSM remember to execute the operation 1+2?




- System initialization
- The first operand
- The operator
- The second operand
- The result
- Which of them had been entered yet

**Try one on your own:
Draw a state diagram for**


$$2+2+5=$$

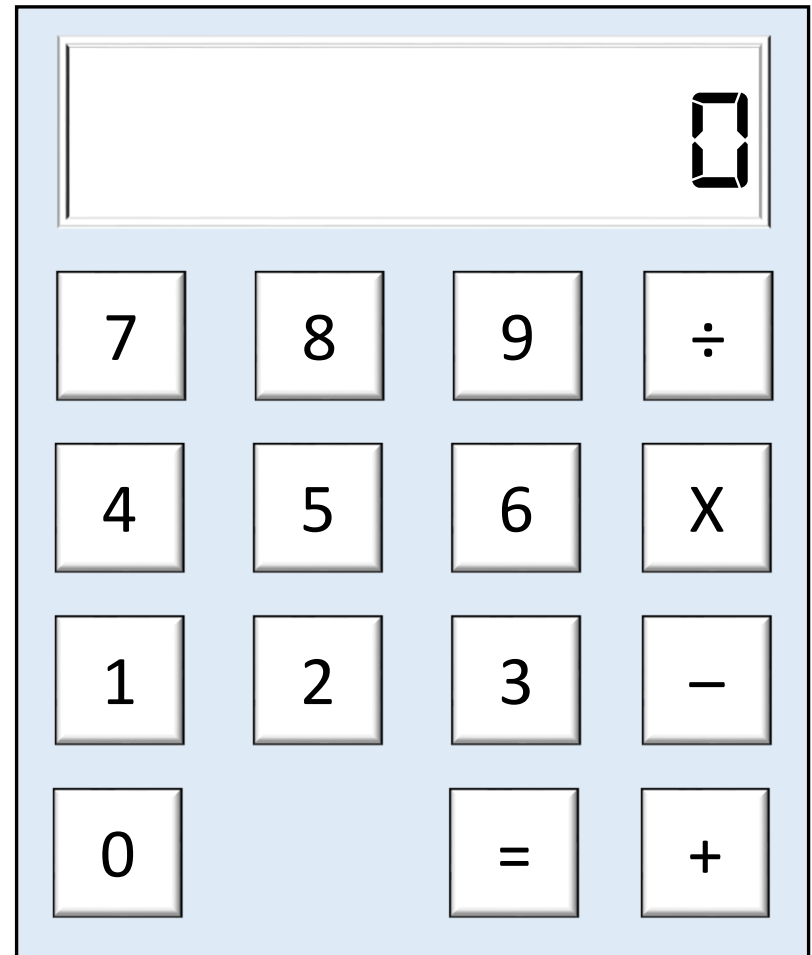

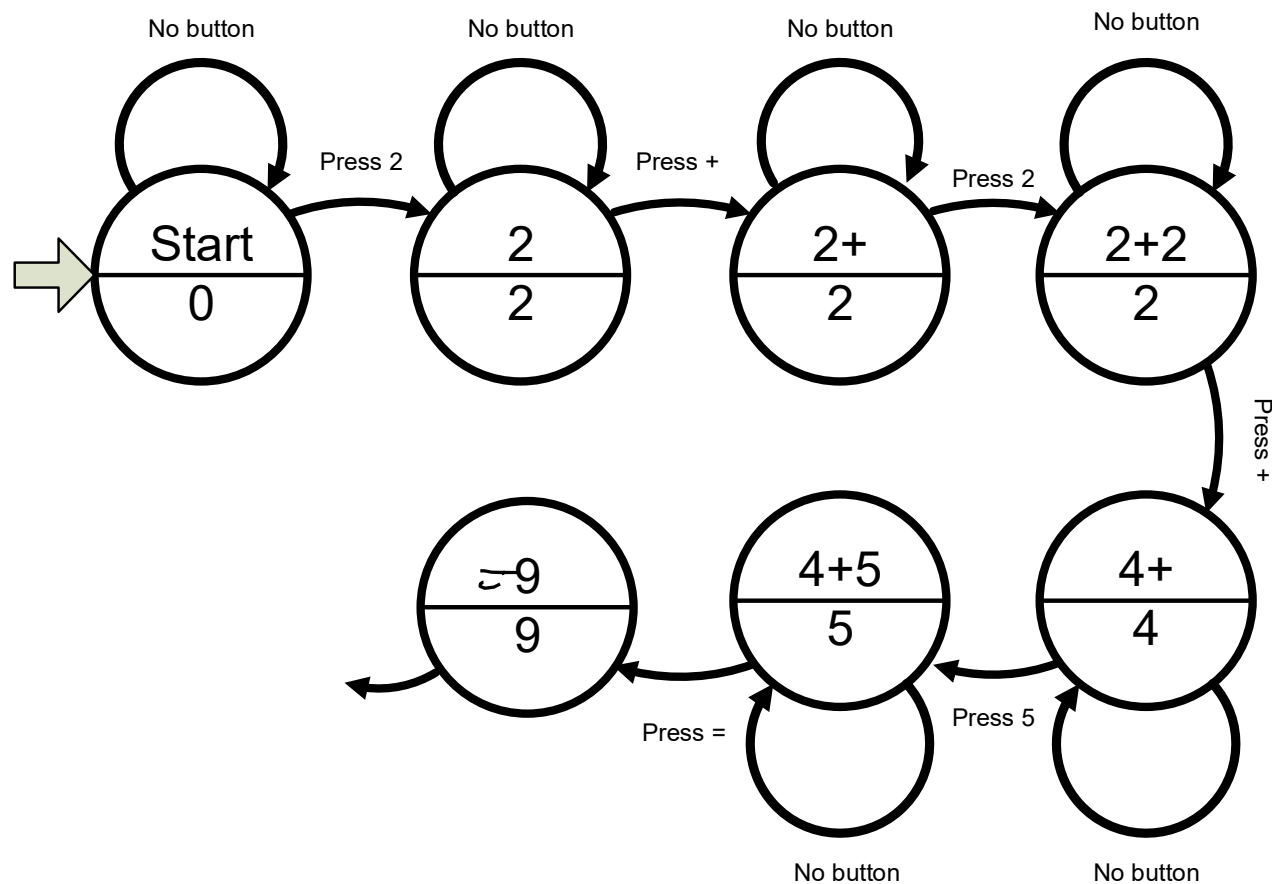
Try one on your own: Draw a state diagram for $2+2+5$



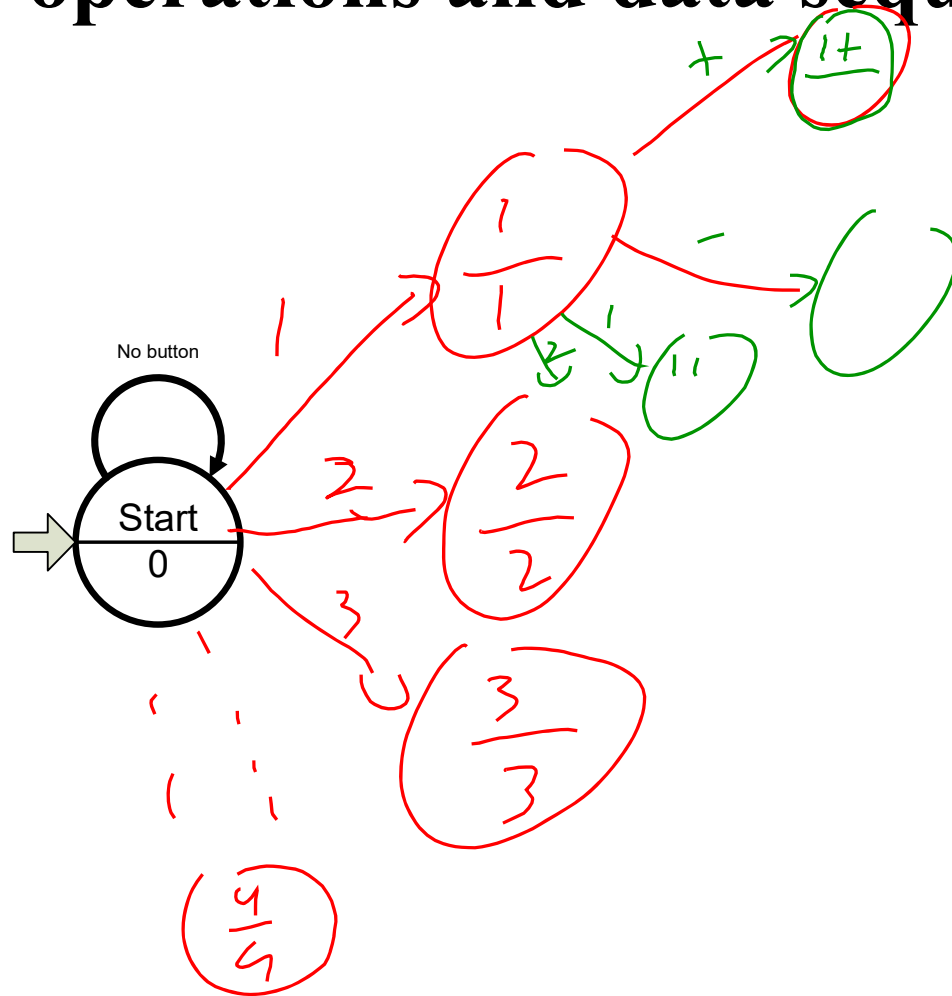Let's build a FSM that allows for several operations and data sequences



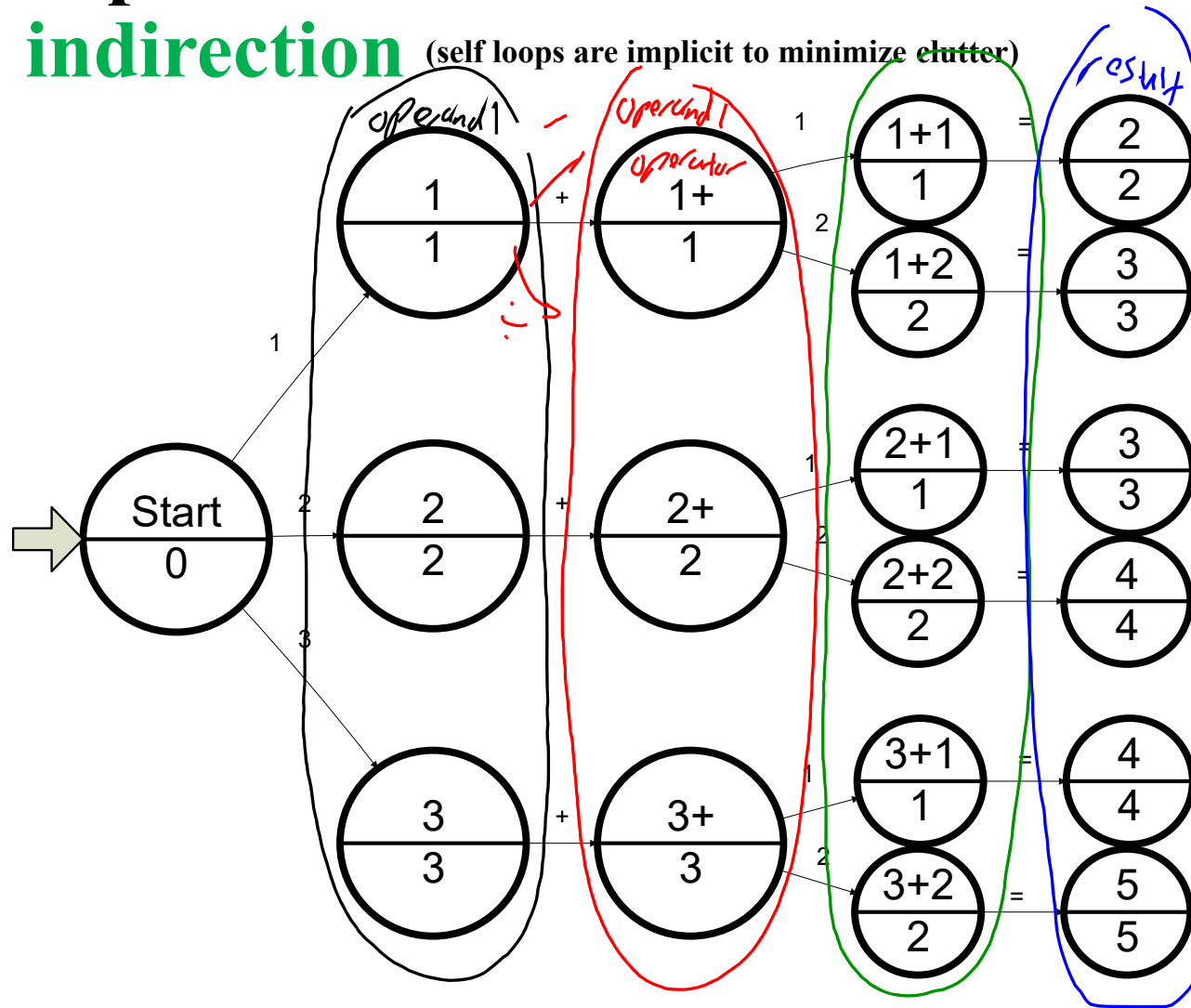
Separate the **data** from the **control** using **indirection** (self loops are implicit to minimize clutter)




operand1, operand2,
operator, and result
are data

Start state and
"which data has been
entered" are control


Offload **data** onto external variables

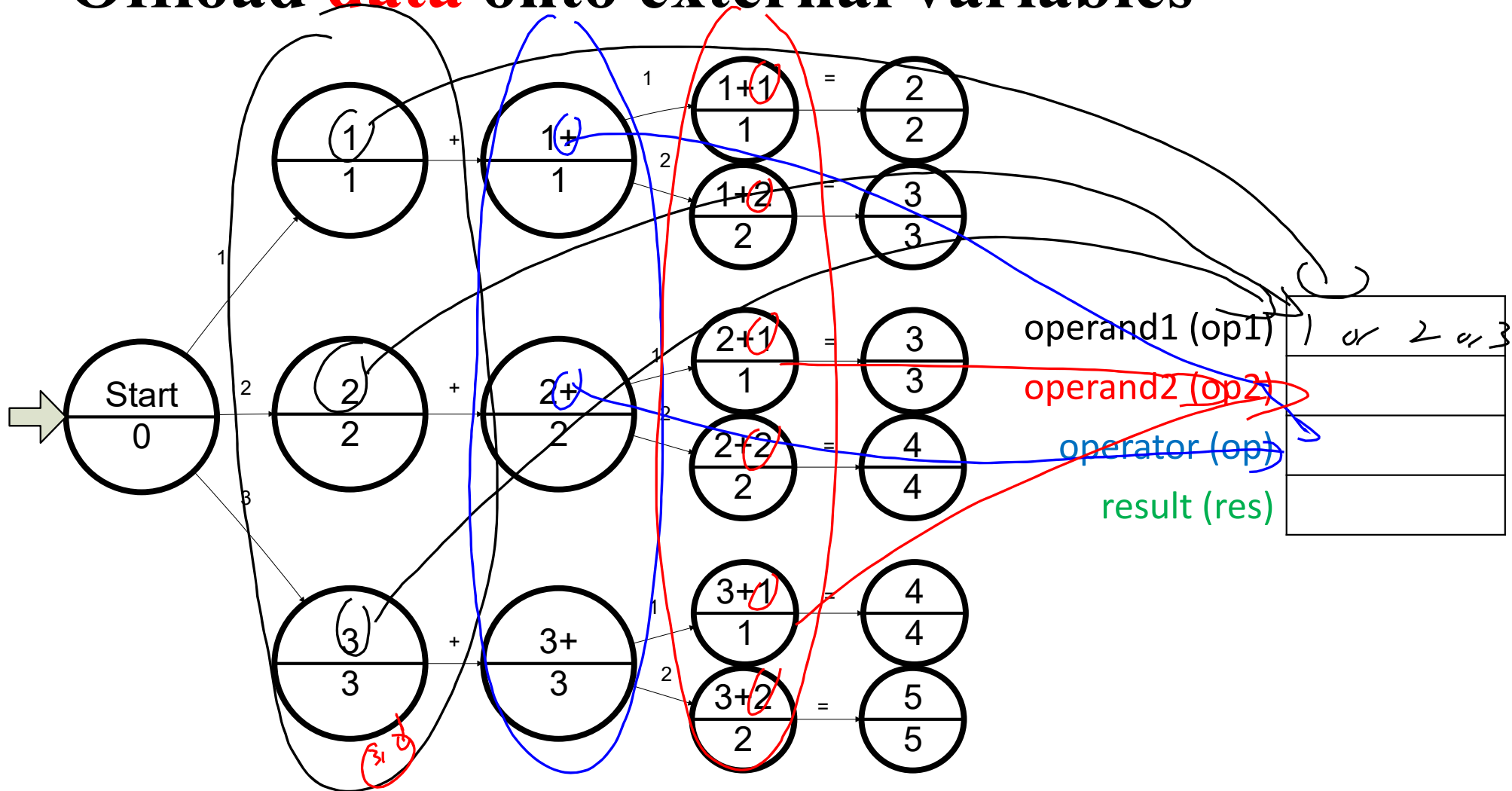


Our generalized calculator FSM so far

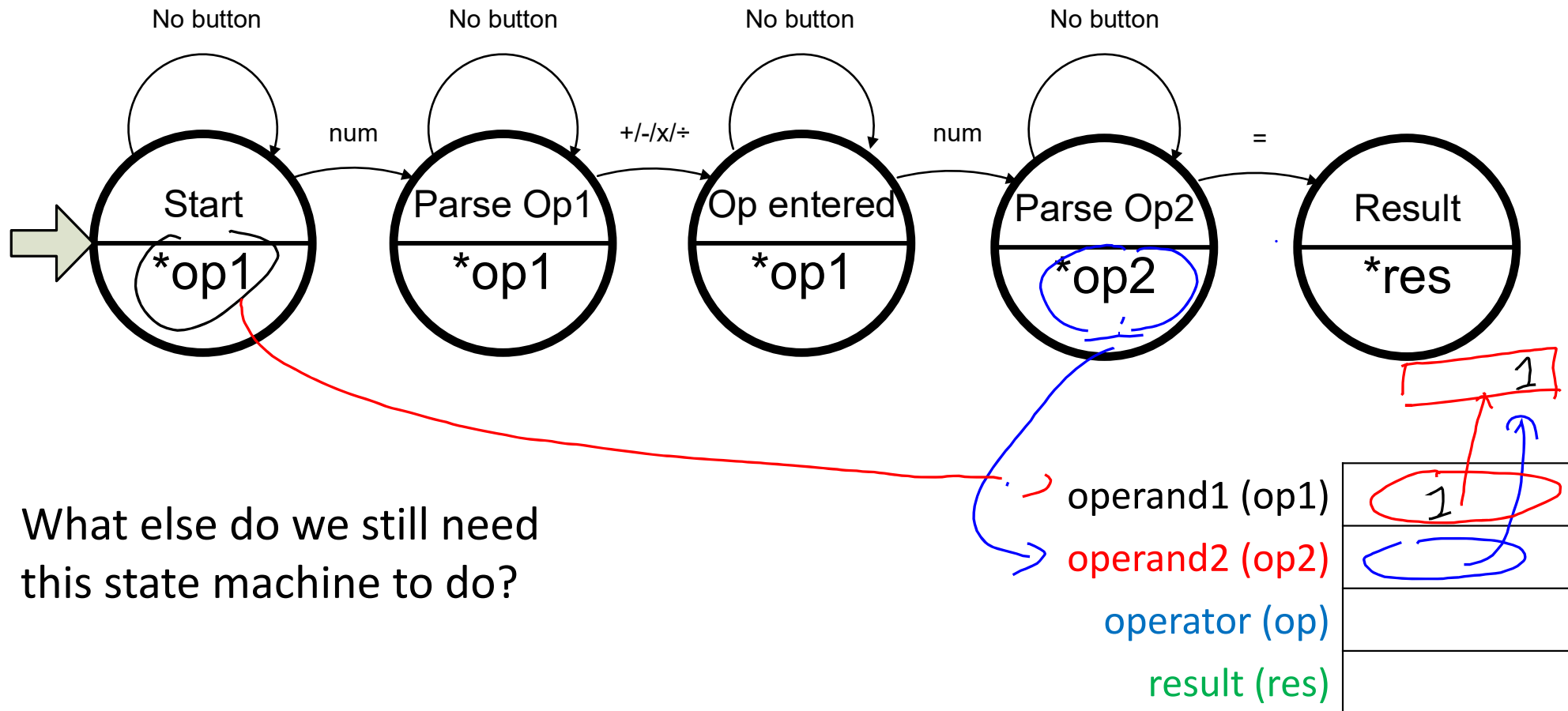

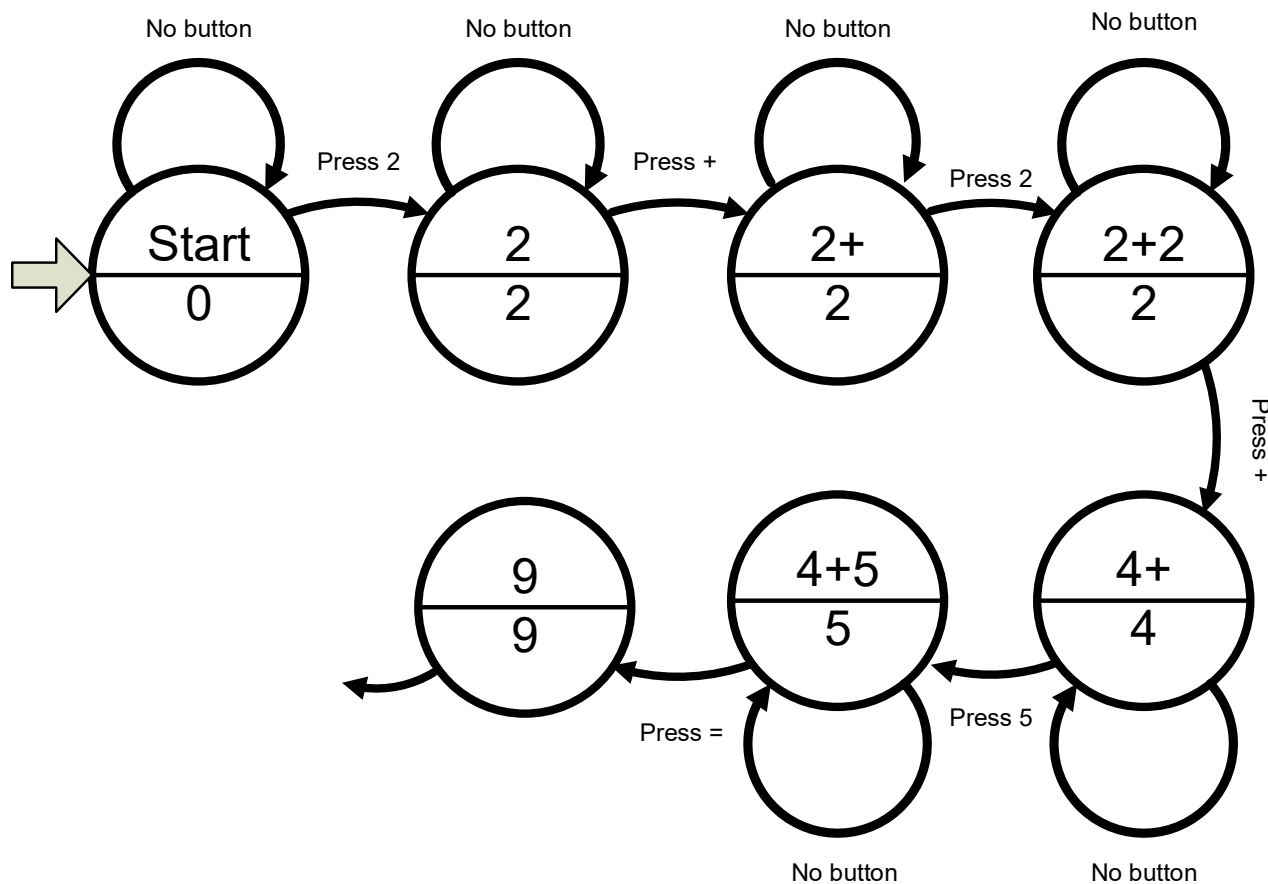Note that the 2+ and 4+ states are functionally similar



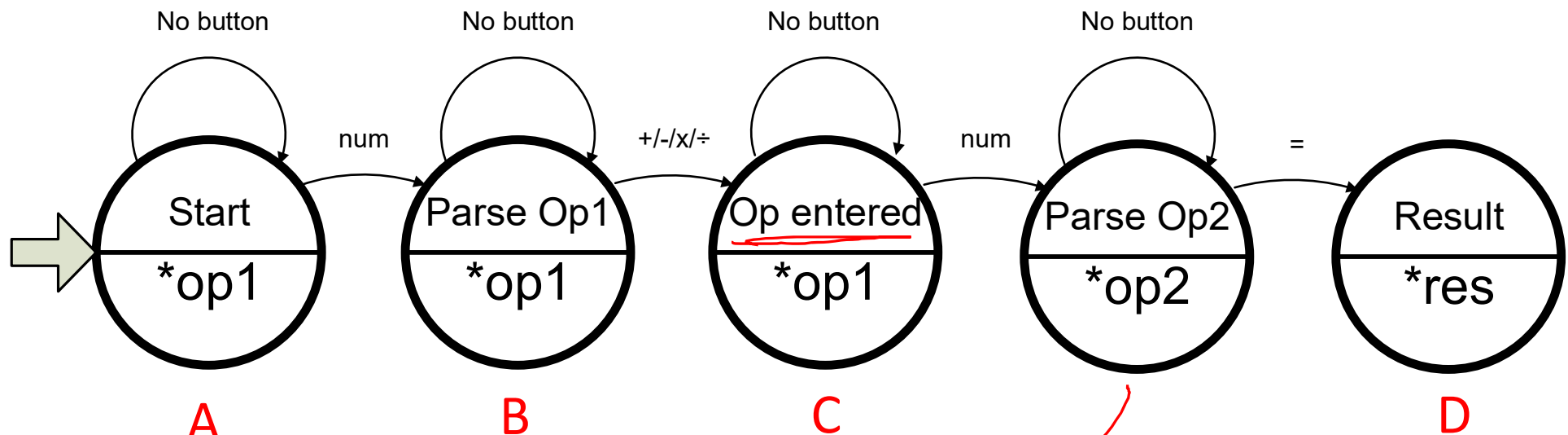What is the next state when an operator is pressed during the *Parse Op2* state?



operand1 (op1)


operand2 (op2)

operator (op)


result (res)

Handwritten red text: ? + / - / x / ÷ .


What happens after we have a result?

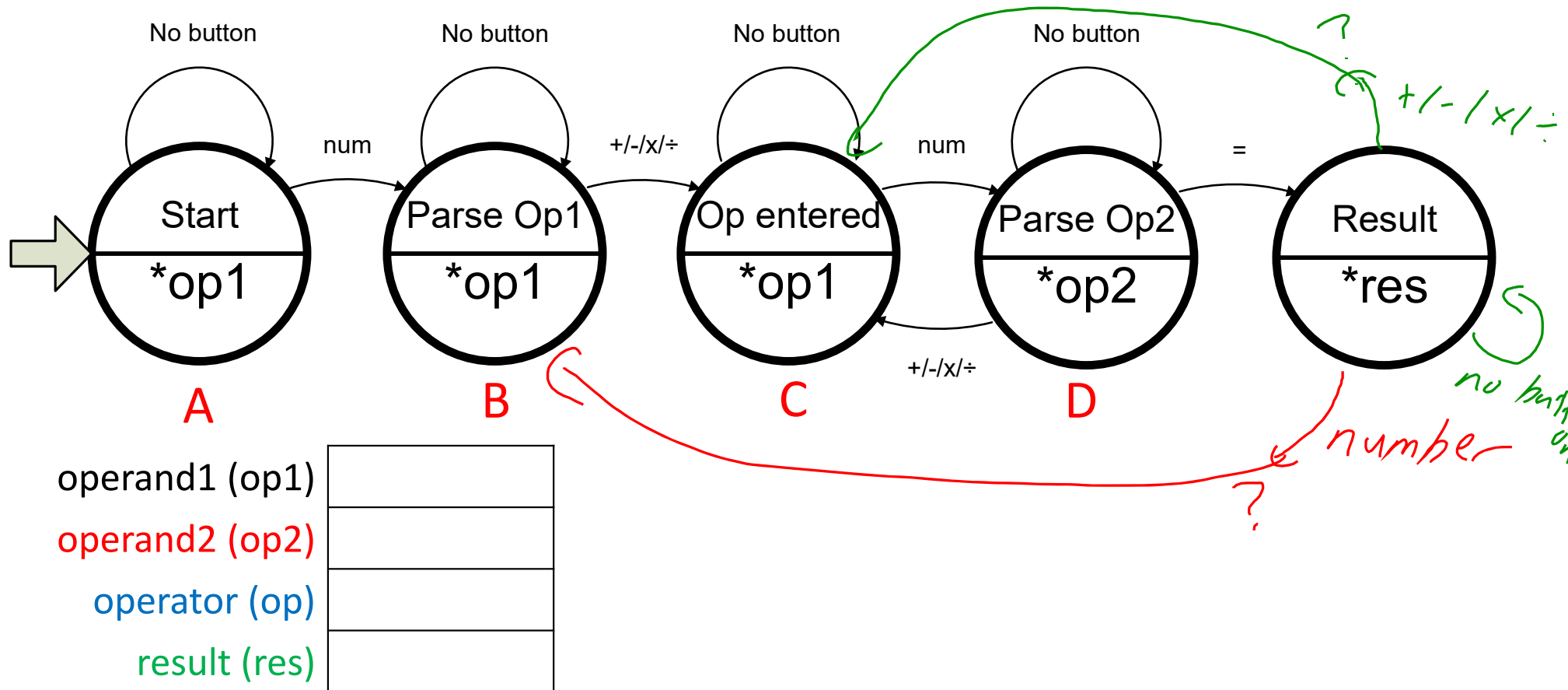

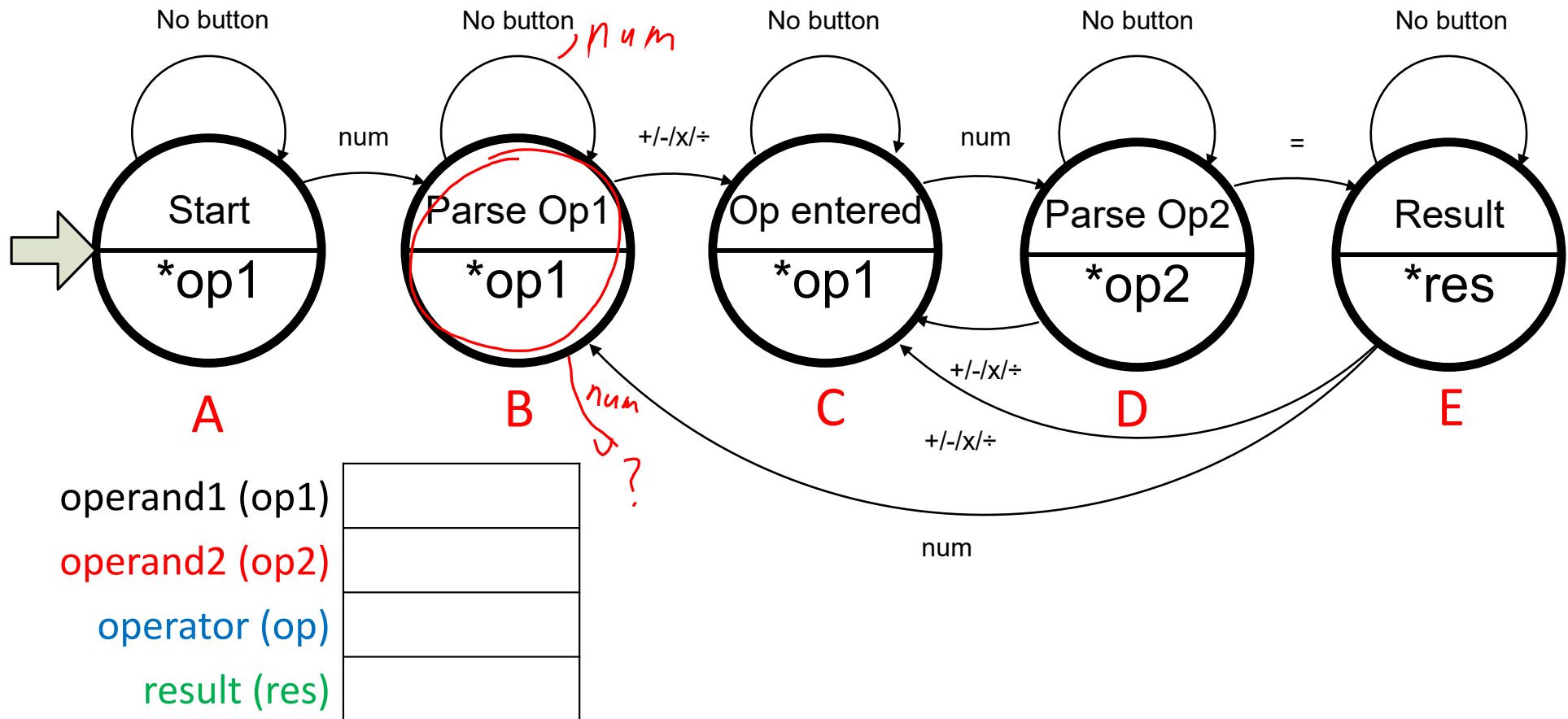
What happens if our operands have multiple digits?




Our generalized calculator FSM

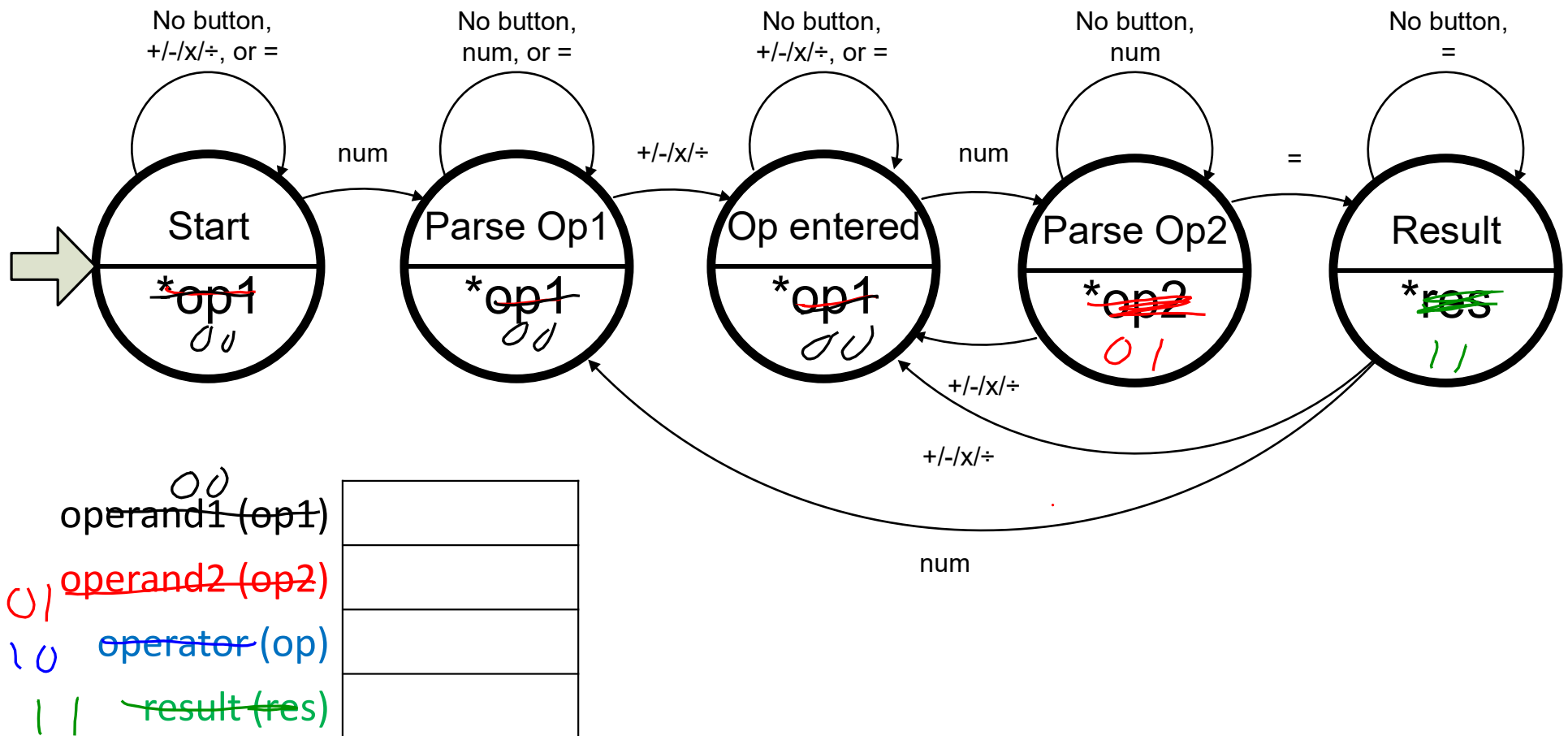

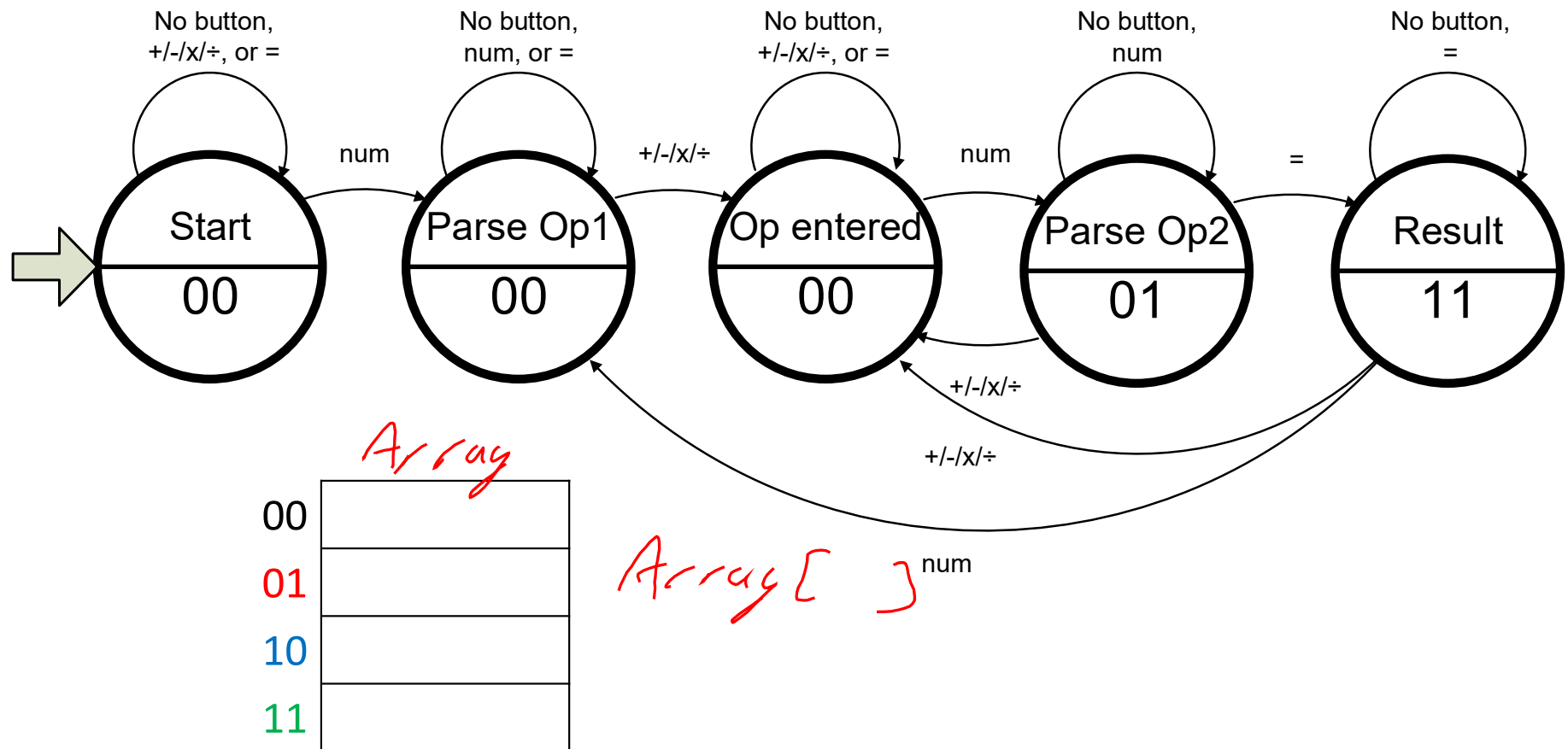To implement **indirection**, treat the variables as indices in an array



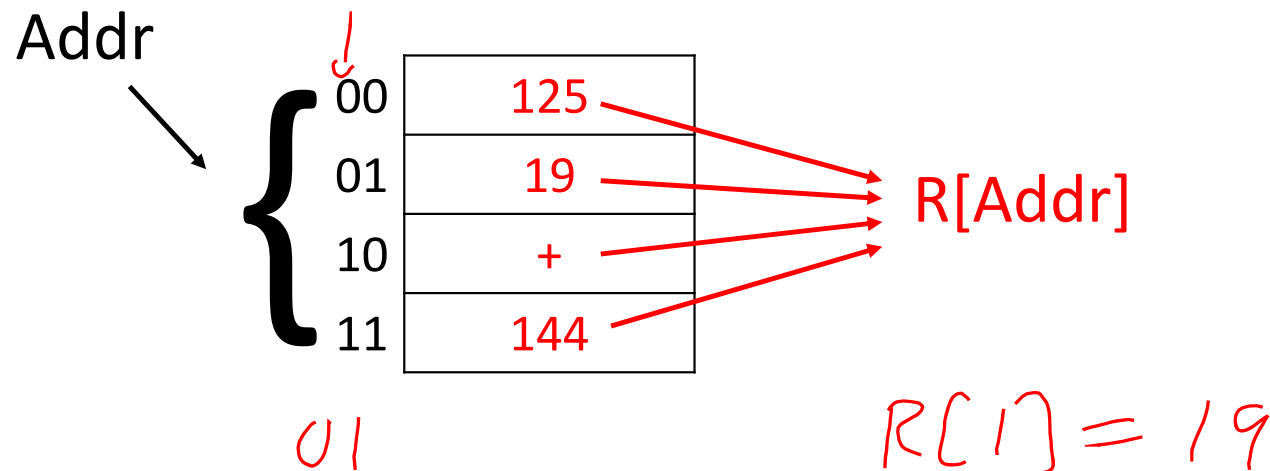
Use brackets to indicate the data stored at an address in an array (a.k.a. a register file)




How many bits should be stored at each address?

- A) 8
- B) 27
- C) 48
- D) 108
- E) 256

00	
01	
10	
11	

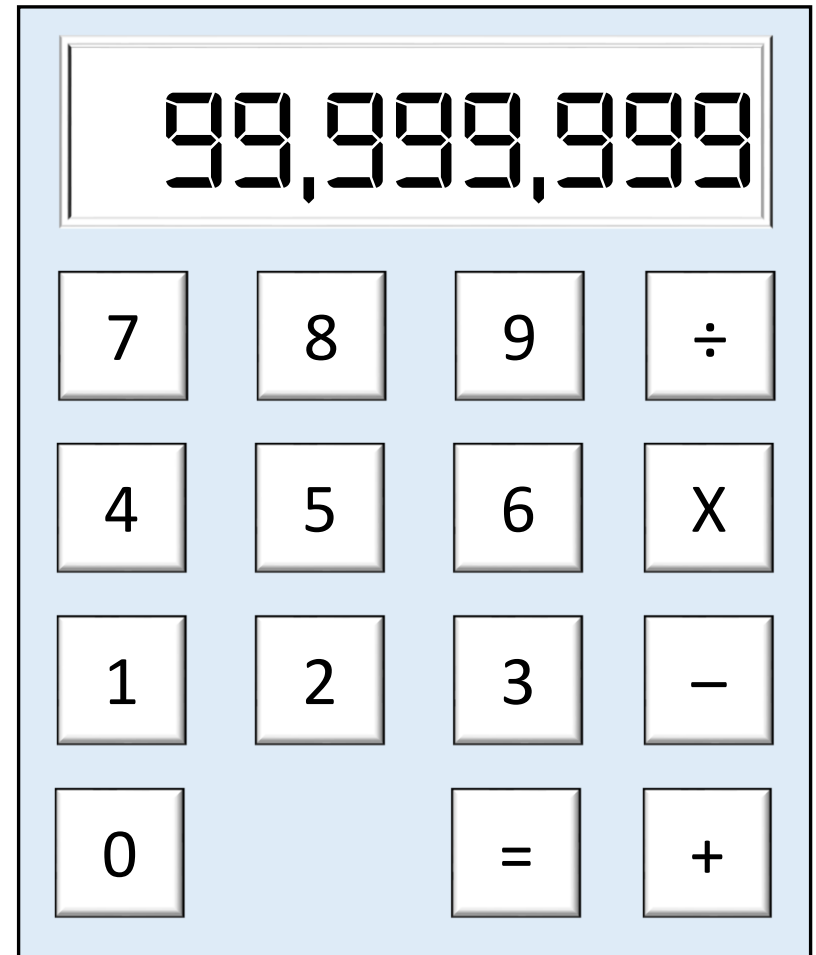

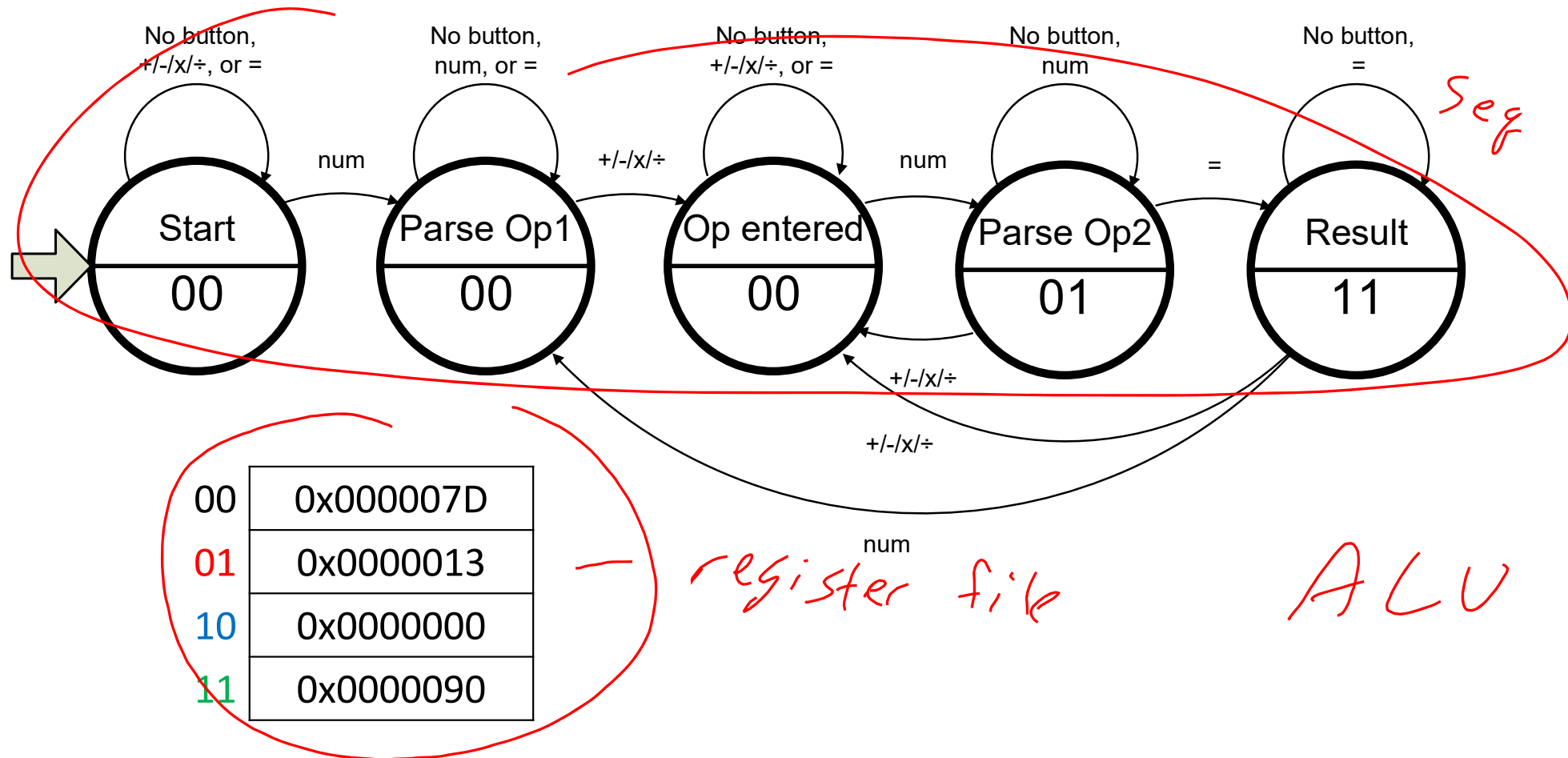What components do I need in a circuit to implement this FSM?



Use the FSM and system input to **control** the register file and ALU (the **datapath**)

