
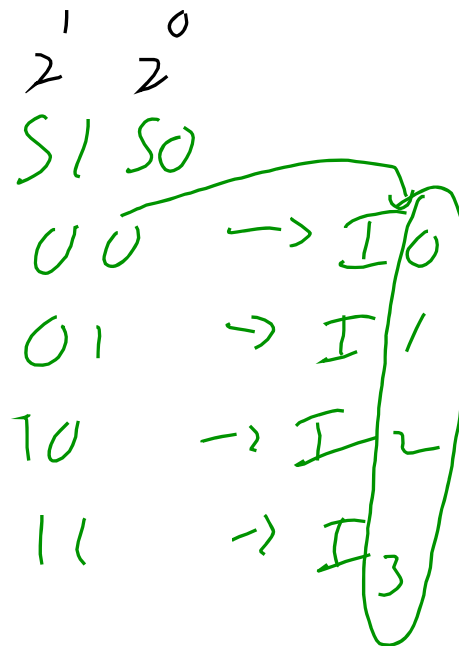


Mux Hierarchical Design (more inputs)

- How do we build a mux with 4 inputs?

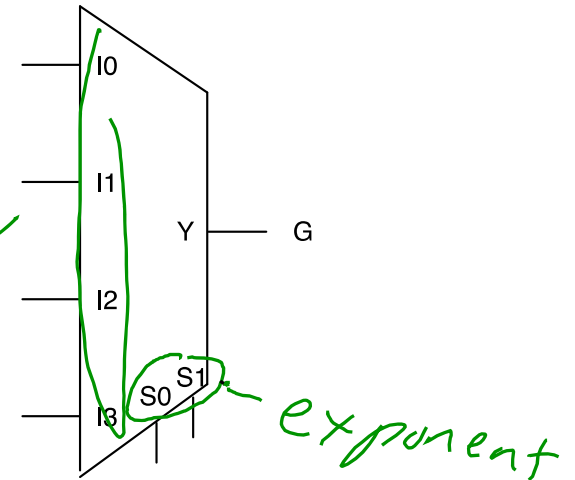

decimal




iclicker®

- | | |
|----|--------|
| A: | S_0 |
| B: | S_1 |
| C: | Either |

Mux Hierarchical Design (more inputs)

- How do we build a mux with 4 inputs?

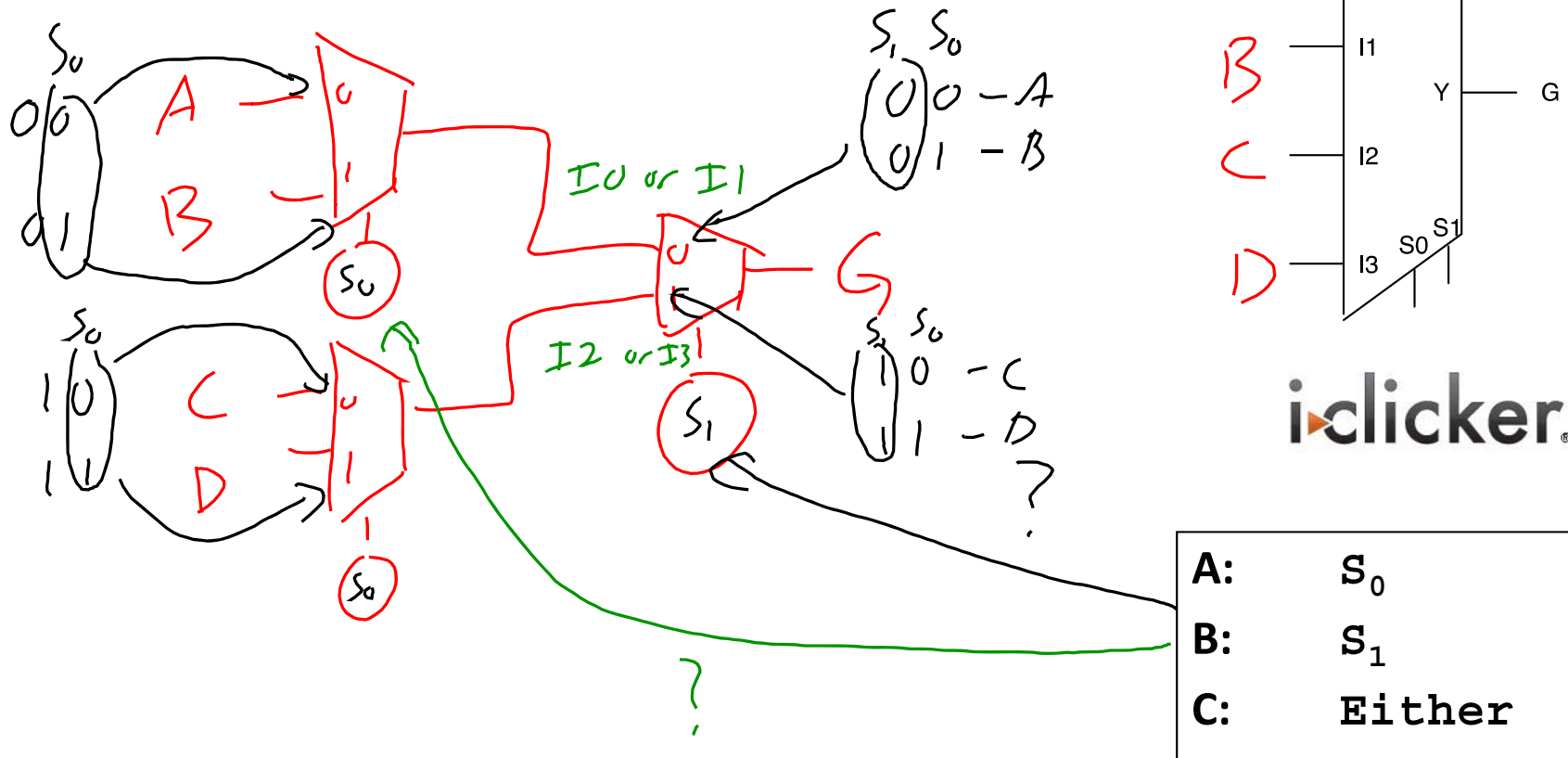

Building an ALU (Part 2):

Happy Monday!


Exam 1 covers through
today's lecture + delay
2 parts: short answer + verilog

State – the central concept of computing

Computer can do 2 things

1) Store state

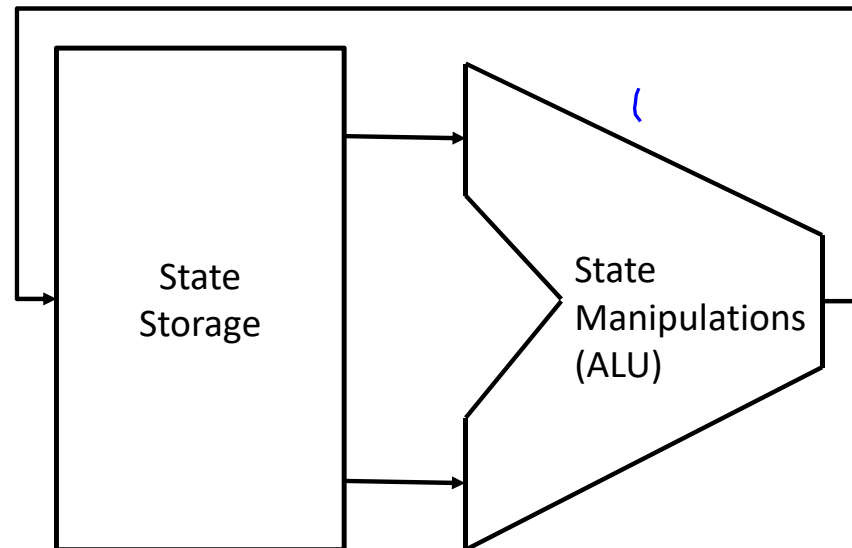
2) Manipulate state (Combine arithmetic and logical operations into one unit)



Today's lecture

- We'll finish the 32-bit ALU today!
 - 32-bit ALU specification
- Complete 1-bit ALU
- Assembling them to make 32-bit ALU
- Handling flags:
 - zero, negative, overflow

A specification for a 32-bit ALU

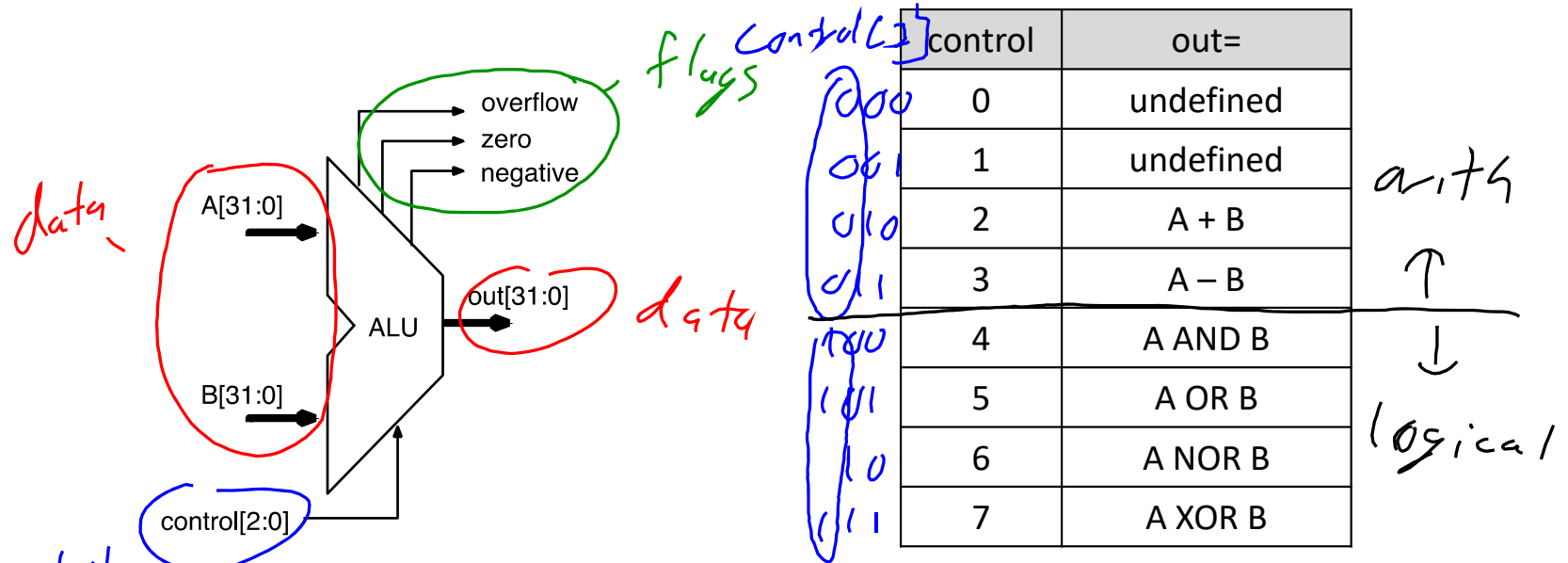


```

module alu32(out, overflow, zero, negative, A, B, control);
    output[31:0] out;
    output overflow, zero, negative;
    input [31:0] A, B;
    input [2:0] control;
  
```

Did overflow occur?
 Is the output equal to zero?
 Is the output negative?

Use a modular 1-bit ALU to build 32-bit ALU

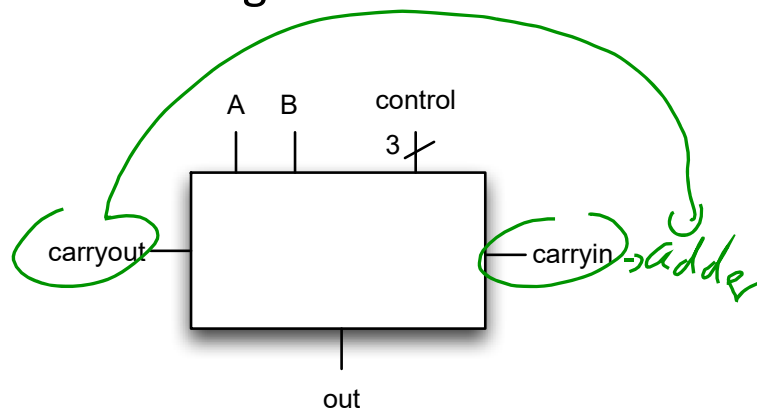- Previously we showed 1-bit adder/subtractor, 1-bit logic unit
 - Time to put them together.




control	out _i =
0	undefined
1	undefined
2 <i>010</i>	<i>Control[0]</i> $A_i + B_i$
3 <i>011</i>	<i>Control[0]</i> $A_i - B_i$
4 <i>100</i>	$A_i \text{ AND } B_i$
5 <i>101</i>	$A_i \text{ OR } B_i$
6 <i>110</i>	$A_i \text{ NOR } B_i$
7 <i>111</i>	$A_i \text{ XOR } B_i$

```

module alu1(out, carryout, A, B, carryin, control);
    output      out, carryout;
    input       A, B, carryin;
    input [2:0] control;
    
```

Addition + Subtraction in one circuit (1-bit Arithmetic Unit)

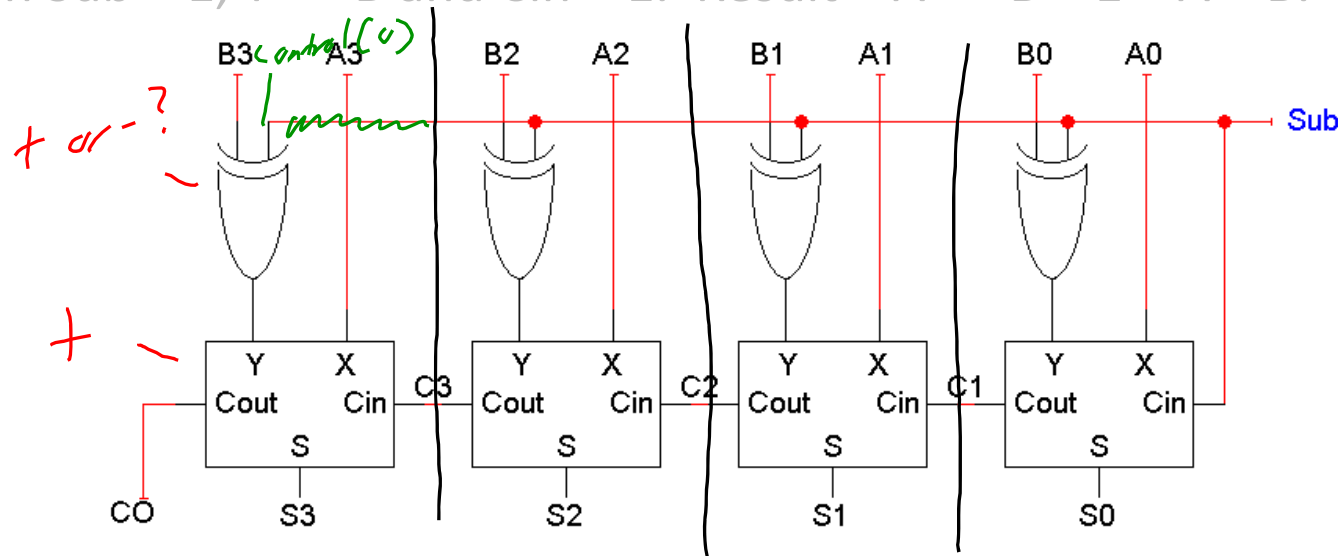
- When $\text{Sub} = 0$, $Y = B$ and $\text{Cin} = 0$. Result = $A + B + 0 = A + B$.
- When $\text{Sub} = 1$, $Y = \sim B$ and $\text{Cin} = 1$. Result = $A + \sim B + 1 = A - B$.



- Which parts belong in inside the 1-bit ALU?
A) the Full Adder, B) the XOR gate, C) Both, D) Neither

Addition + Subtraction in one circuit (1-bit Arithmetic Unit)

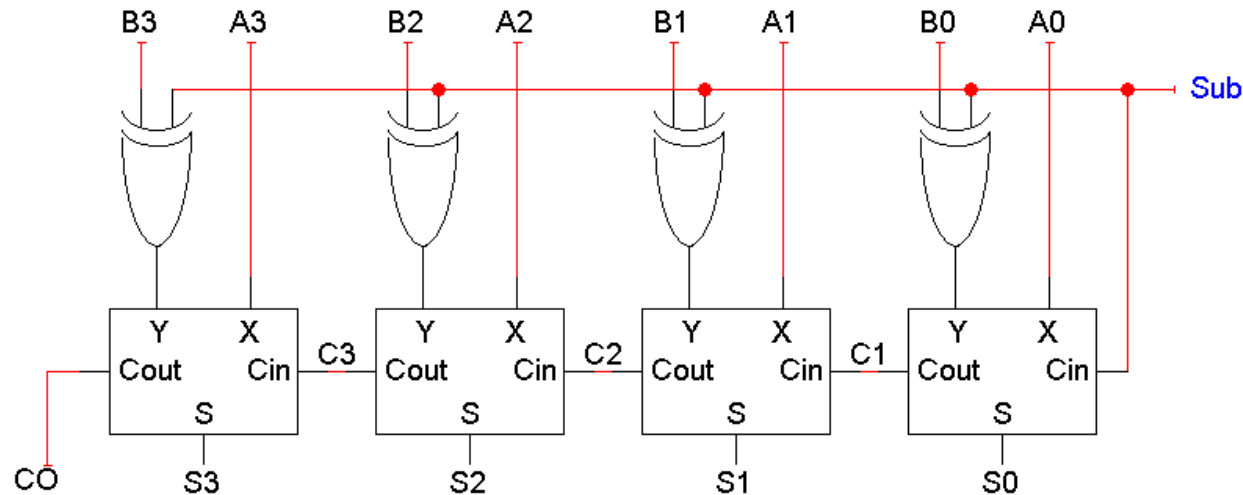
- When $\text{Sub} = 0$, $Y = B$ and $\text{Cin} = 0$. Result = $A + B + 0 = A + B$.
- When $\text{Sub} = 1$, $Y = \sim B$ and $\text{Cin} = 1$. Result = $A + \sim B + 1 = A - B$.



- What should we do with the full adder's Cin input?
A) Connect to Sub, B) Connect to 1-bit ALU's carryin

Addition + Subtraction in one circuit (1-bit Arithmetic Unit)

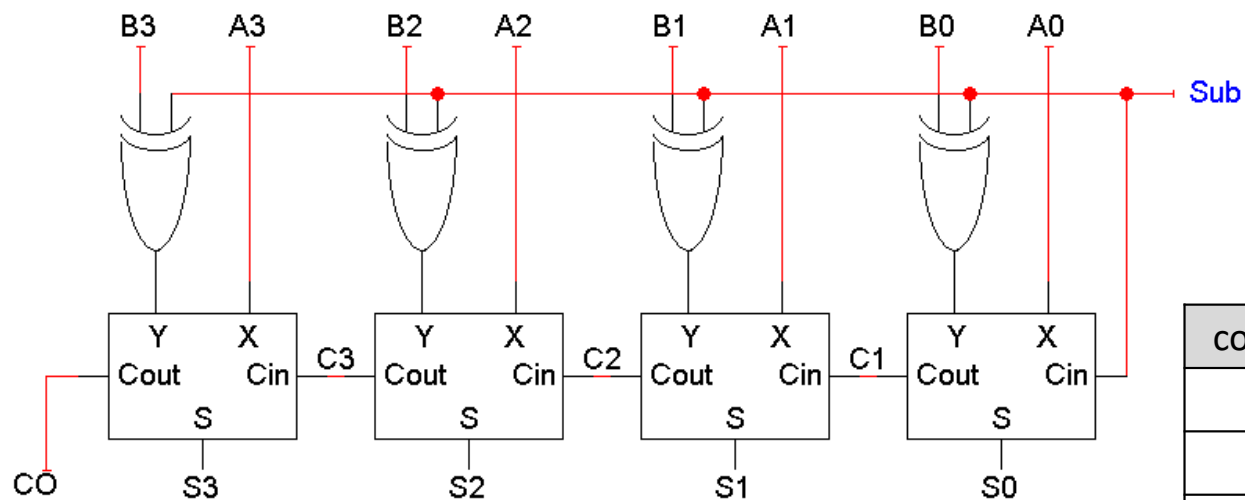
- When $\text{Sub} = 0$, $Y = B$ and $\text{Cin} = 0$. Result = $A + B + 0 = A + B$.
- When $\text{Sub} = 1$, $Y = \sim B$ and $\text{Cin} = 1$. Result = $A + \sim B + 1 = A - B$.




control	out=
0	undefined
1	undefined
2	$A + B$
3	$A - B$

- Where will the “Sub” signal come from?

Complete 1-bit ALU

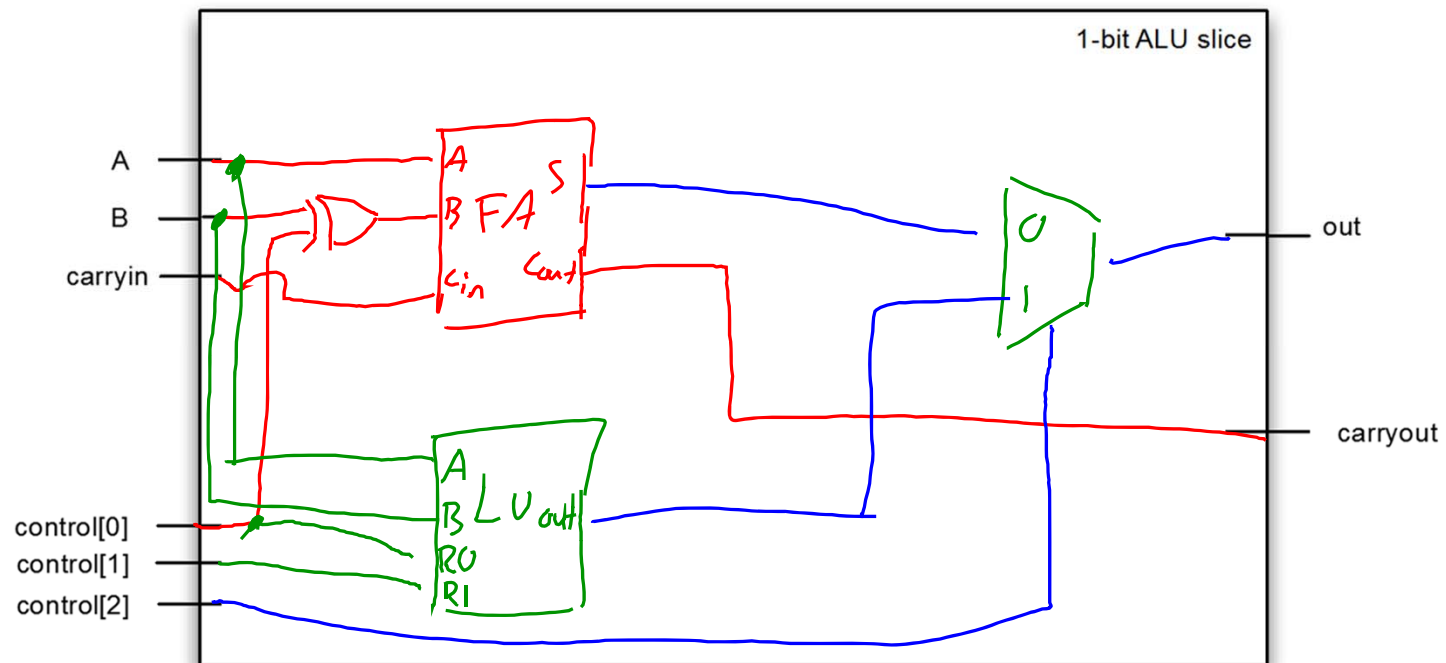


Complete 1-bit Logic Unit

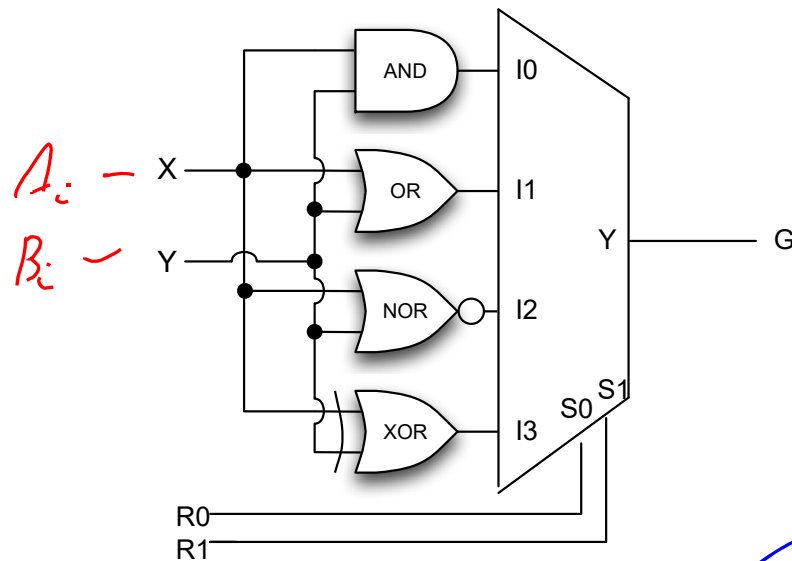


R_1	R_0	Output
0	0	$G_i = X_i Y_i$
0	1	$G_i = X_i + Y_i$
1	0	$G_i = (X_i + Y_i)'$
1	1	$G_i = X_i \oplus Y_i$

- What should the control inputs (R0, R1) connect to? *Control [1:0]*
- How do we select between the adder and the logic unit? *Control [2]*
- How do we control the selection?

Complete 1-bit ALU

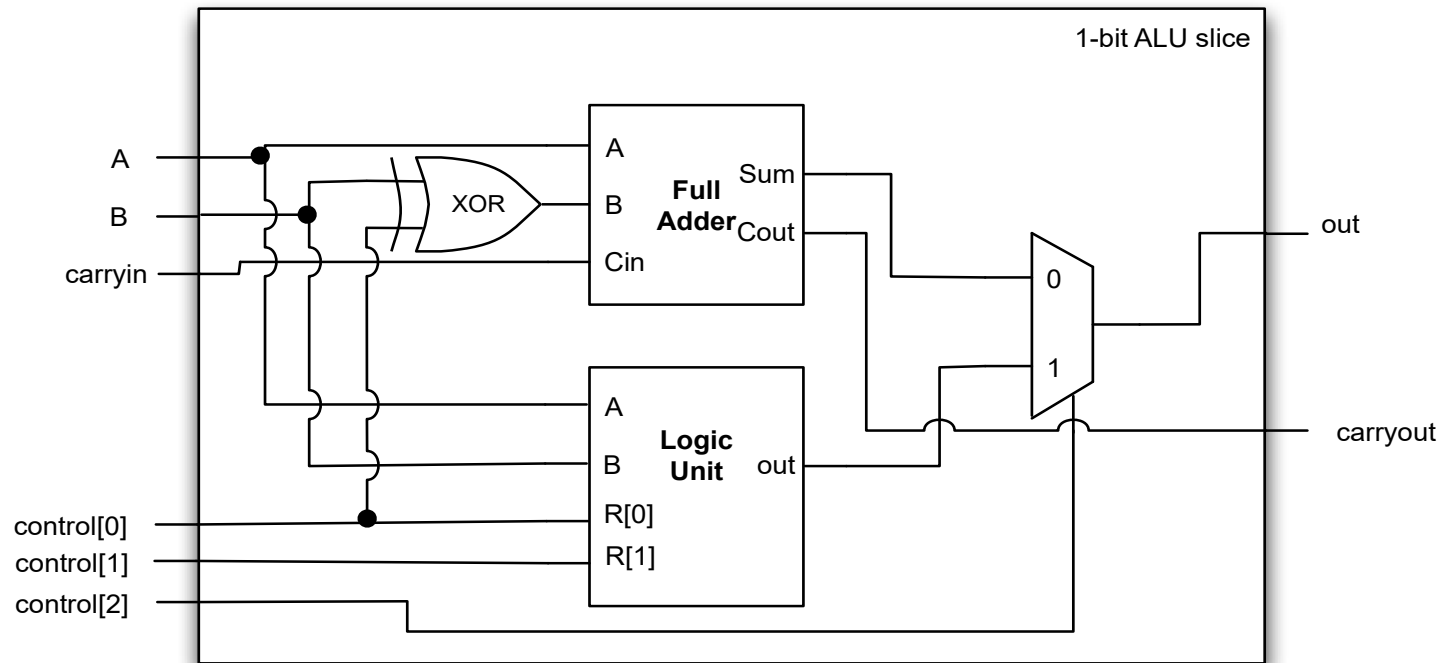

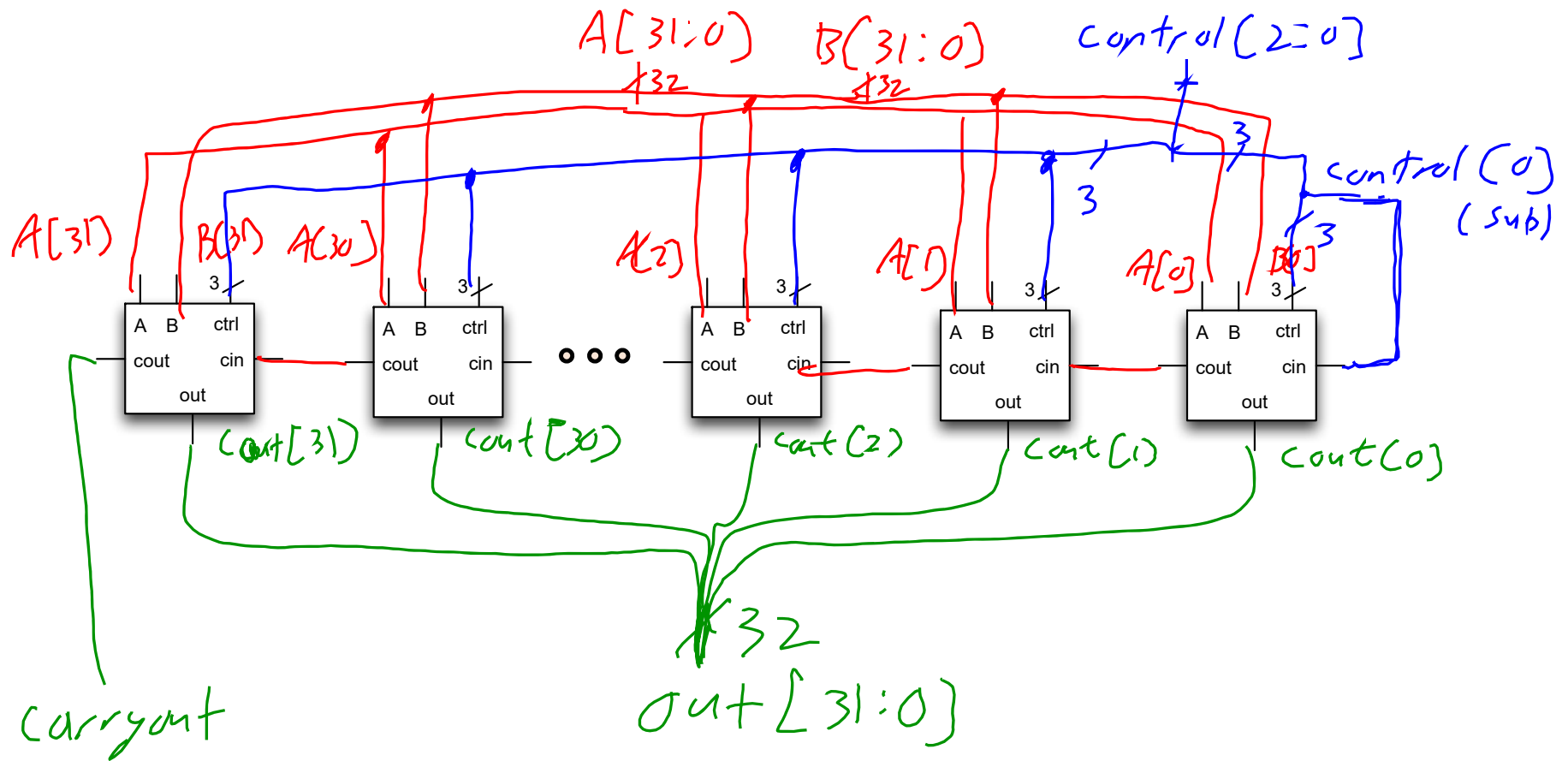Connecting 1-bit ALUs \rightarrow 32-bit ALU



Flags (overflow, zero, **negative**)

- Let's do negative first; negative evaluates to:

- 1 when the output is negative, and
- 0 when the output is positive or zero


- Negative =
 - a) carryout [30]
 - b) output [30]
 - c) carryout [31]
 - d) output [31]
 - e) control [0]

$$\begin{array}{r} \rightarrow 0011 \quad 3 \\ + 1001 \quad (-7) \\ \hline ? \rightarrow 1100 \quad (-4) \end{array}$$

Flags (overflow, **zero**, negative)

- zero evaluates to:
 - 1 when the output is equal to zero, else 0

■ Zero =

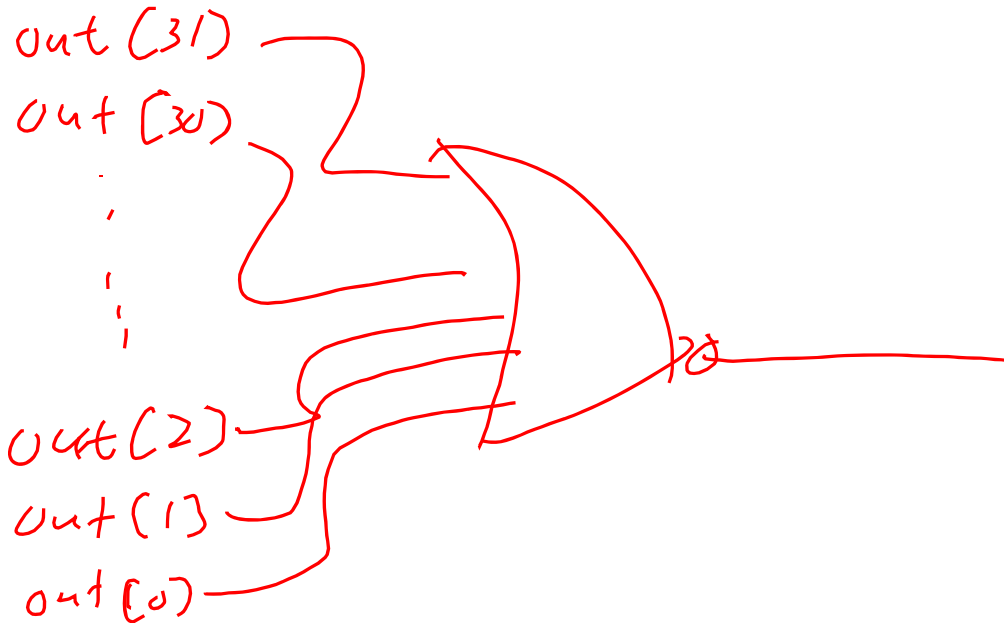

X	y	Zero?
0	0	1
0	1	0
1	0	0
1	1	0

NOR

Flags (**overflow**, zero, negative)

- Overflow (for 2's complement) evaluates to:
 - 1 when the overflow occurred, else 0
 - adding two positive numbers yields a negative number
 - adding two negative numbers yields a positive number
- Consider the adder for the MSB:

X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C _{in}	C _{out}	overflow?
0	0	0
0	1	1
1	0	1
1	1	0

- a) cin[31] NOR cout[31]
- b) cin[31] AND cout[31]
- c) cin[31] OR cout[31]
- d) cin[31] XOR cout[31]
- e) cin[31] NAND cout[31]

 **clicker**®

- Overflow =