

# **Pipelining the MIPS Datapath**

*This week + next week -*

*Pipelining*

*Bring handout back*


# Today's lecture

- Pipeline implementation
  - Single-cycle Datapath
  - Pipelining performance
  - Pipelined datapath
  - Example

# **We have built a **single-cycle implementation** of a subset of the MIPS-based instruction set**

- We have assumed that instructions execute in the same amount of time; this determines the clock cycle time.
- We have implemented the datapath and the control unit.
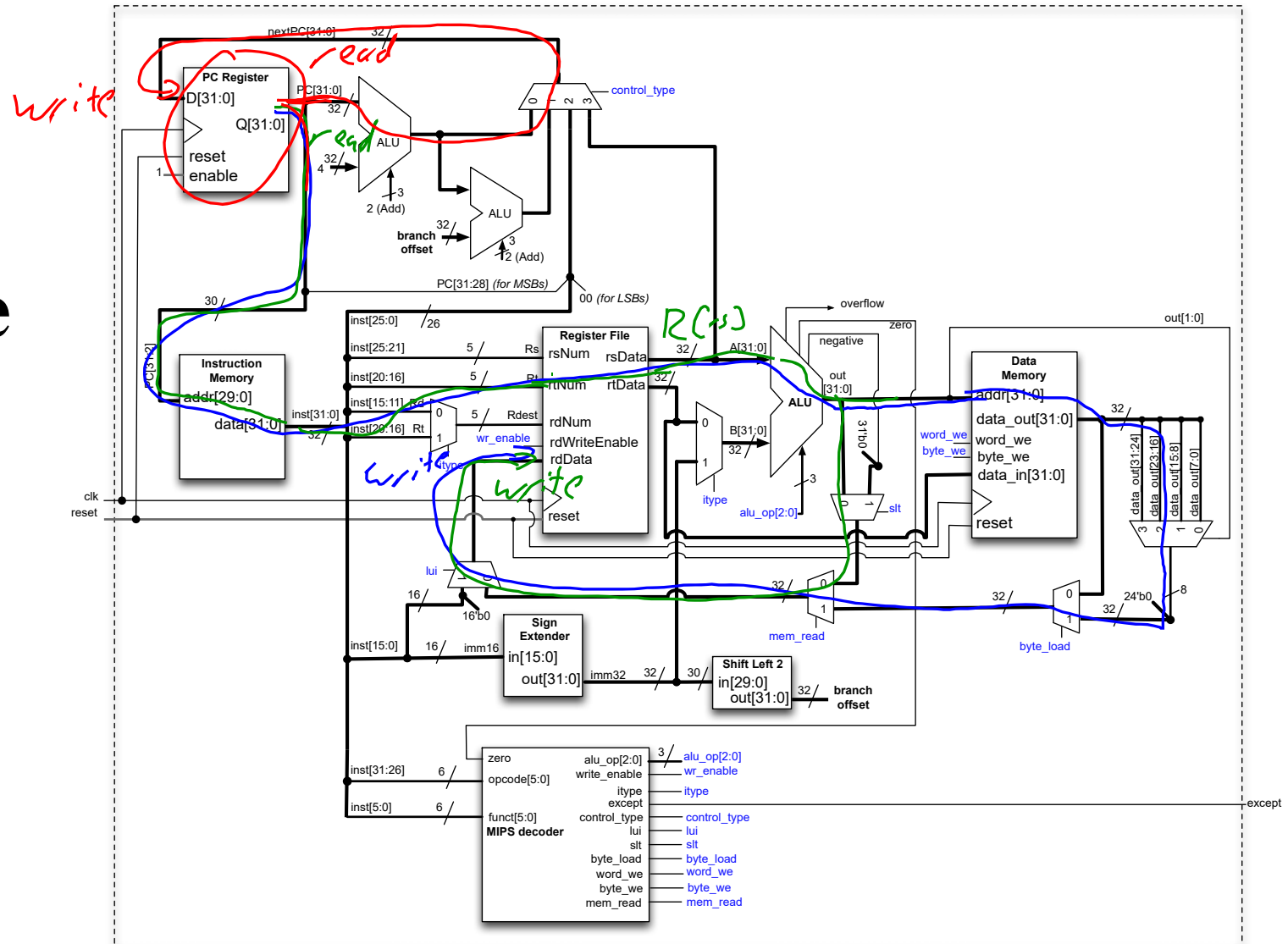
# Refresher: The Full Single-cycle Datapath





**We will use a simplified implementation of MIPS to create a pipelined version**

Arithmetic:    add    sub    and    or    slt

Data            lw    sw  
Transfer:

Control:        beq

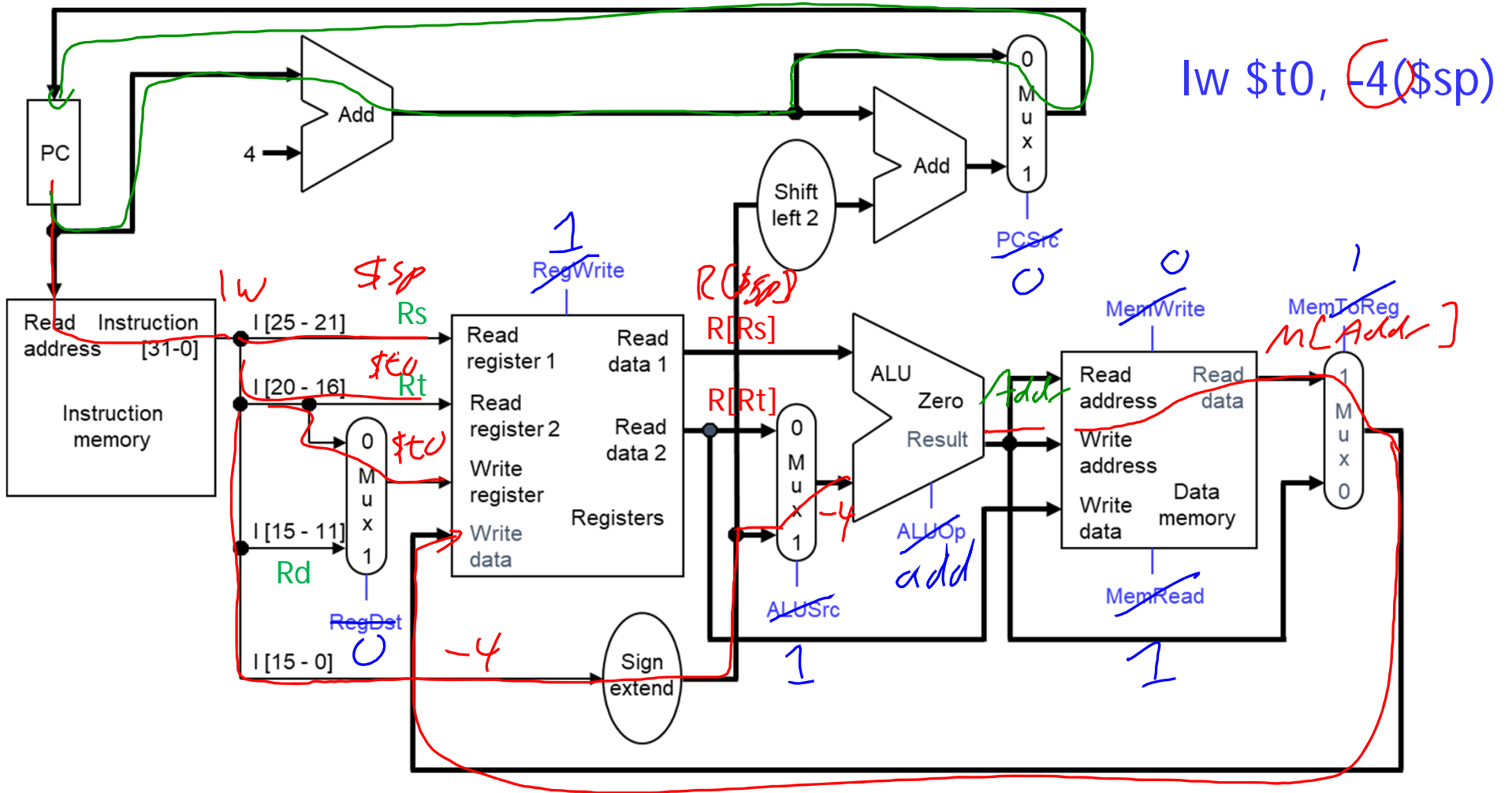


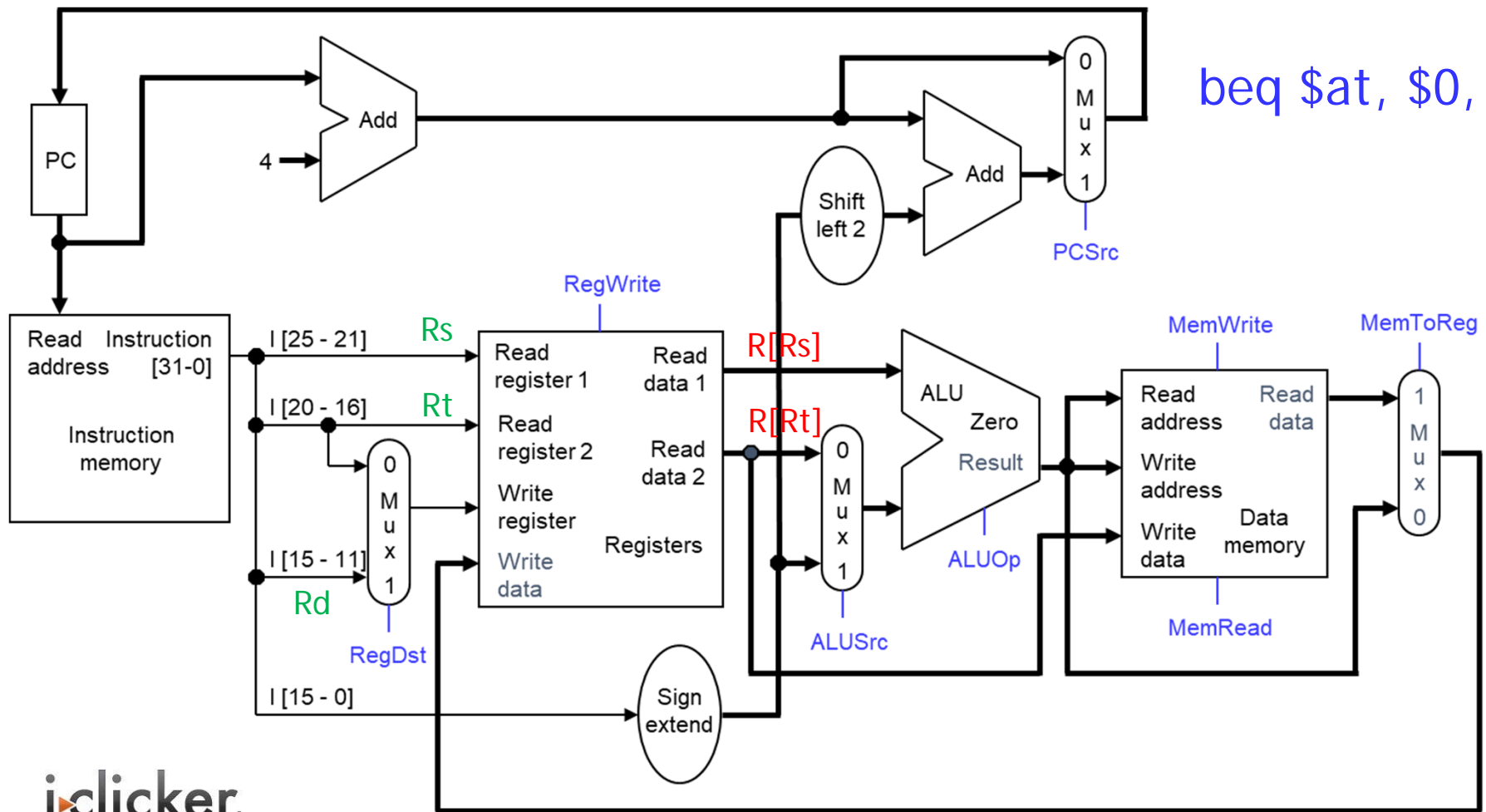

`beq $at, $0, offset`

A) `ALUSrc=0`

B) `ALUSrc=1`

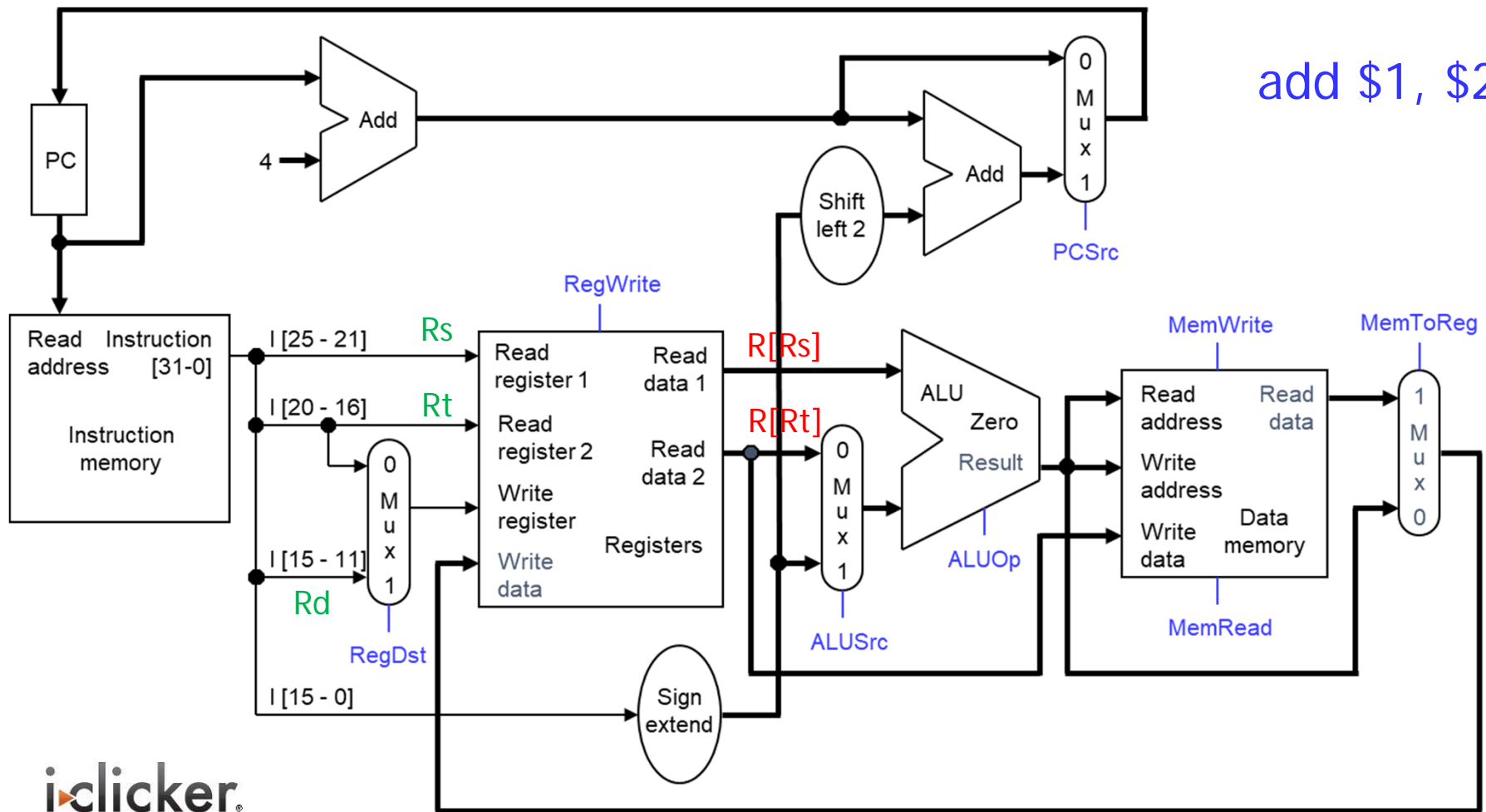


add \$1, \$2, \$3

iclicker®

- A) ALUSrc=0    B) ALUSrc=0    C) ALUSrc=1    D) ALUSrc=1  
       RegDst=0        RegDst=1        RegDst=0        RegDst=1



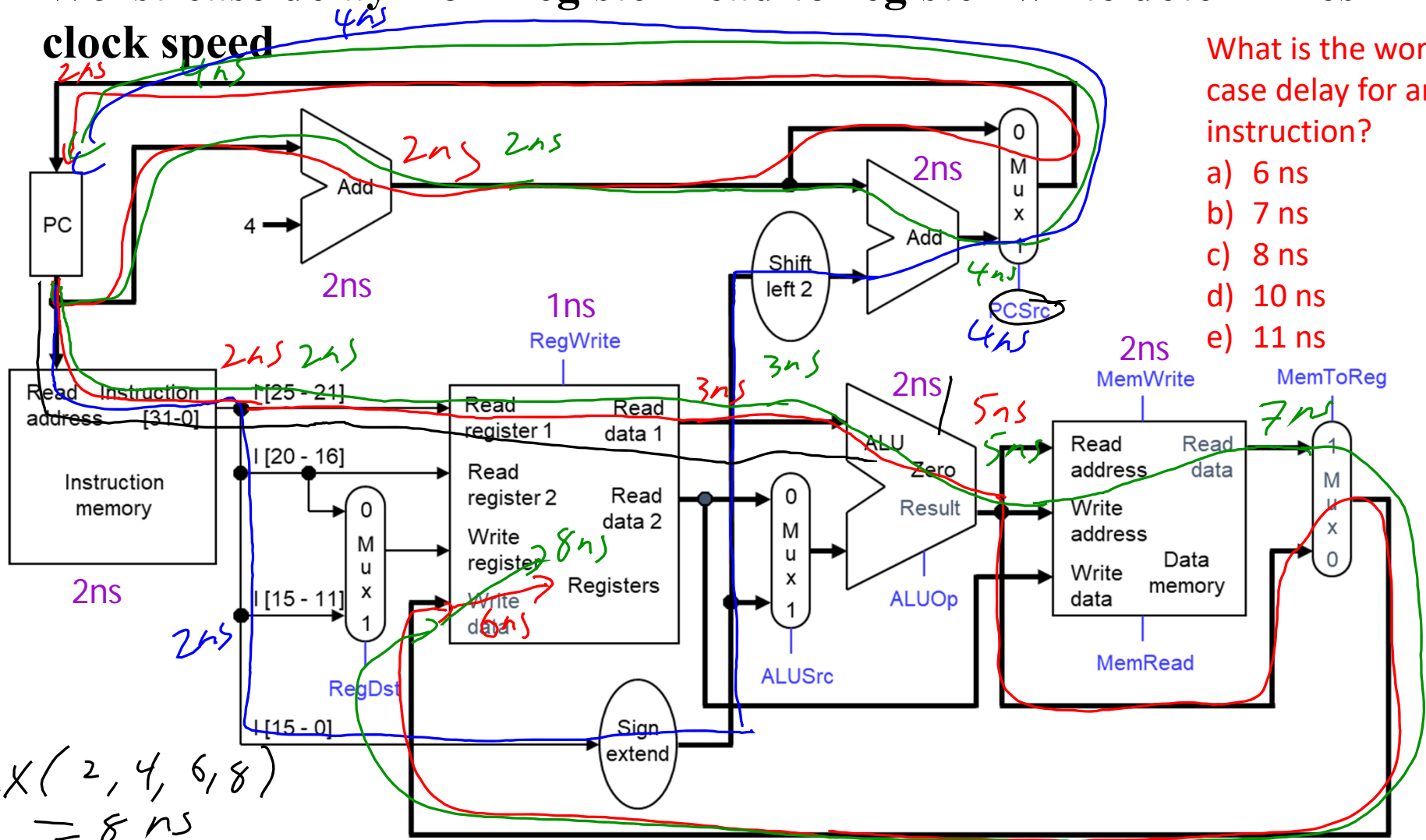**Worst-case delay from register-read to register-write determines clock speed**




What is the worst-case delay for an instruction?


- a) 6 ns
- b) 7 ns
- c) 8 ns
- d) 10 ns
- e) 11 ns

$$\max(2, 4, 6, 8) = 8 \text{ ns}$$
 
# How fast can we clock a pipelined datapath?




# Break datapath into 5 stages

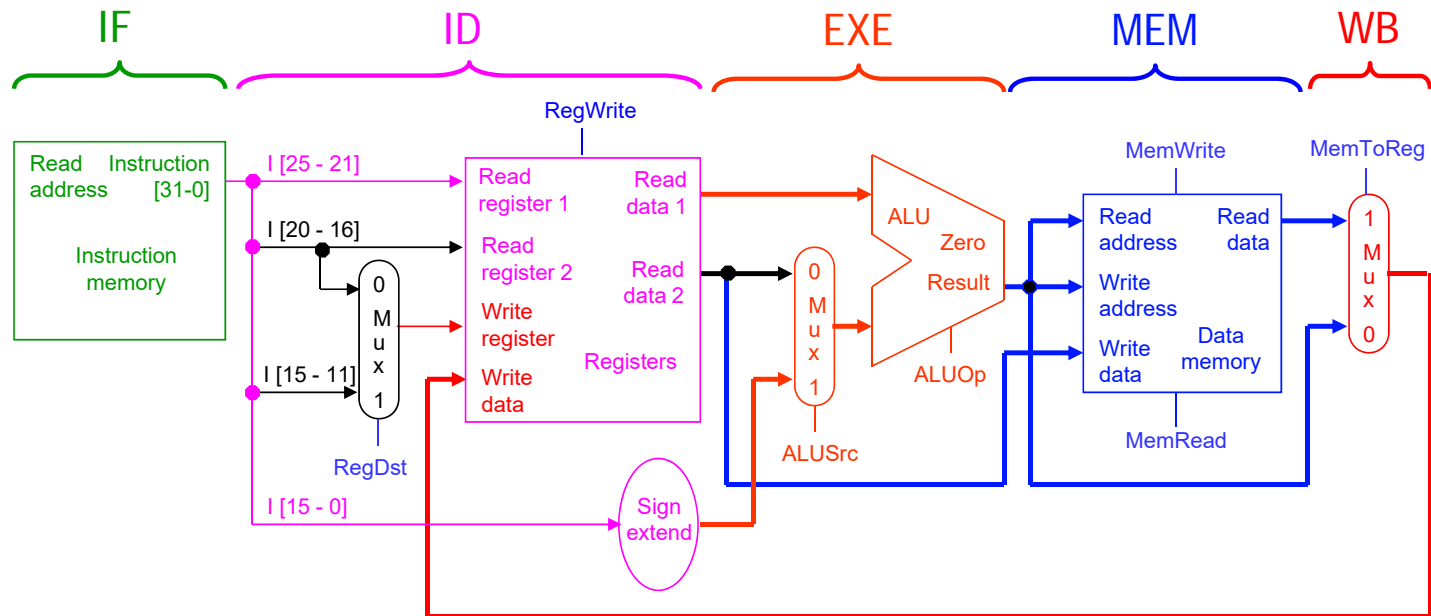

	Clock cycle								
	1	2	3	4	5	6	7	8	9
lw \$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
lw \$t1, 8(\$sp)		IF	ID	EX	MEM	WB			
lw \$t2, 12(\$sp)			IF	ID	EX	MEM	WB		
lw \$t3, 16(\$sp)				IF	ID	EX	MEM	WB	
lw \$t4, 20(\$sp)					IF	ID	EX	MEM	WB

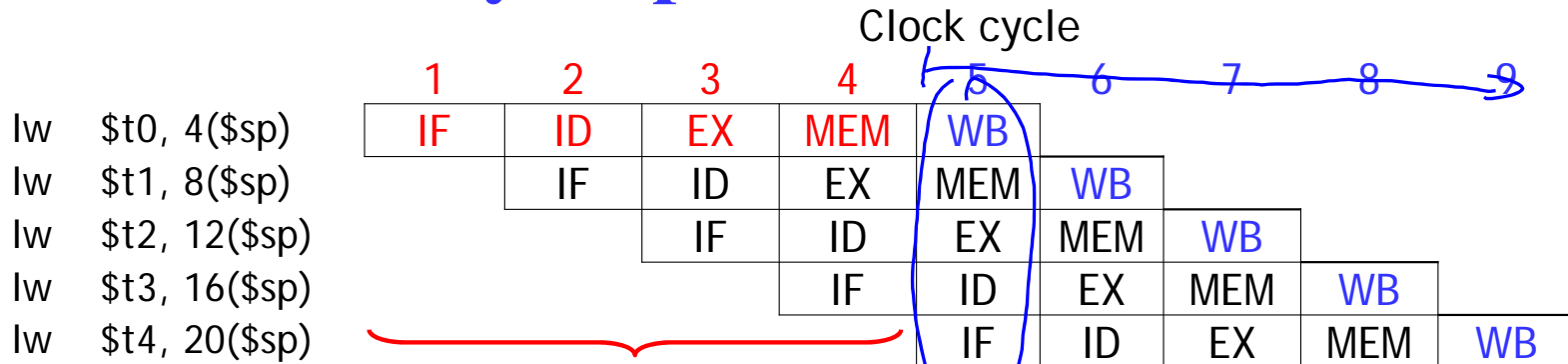
# Ideal pipeline performance is **time to fill the pipeline** + **one cycle per instruction**



- How long for N instructions on pipelined architecture?  $(4 + N) \cdot 2ns = 8 + 2N ns$  (4 + 5) · 2ns = 18ns
- How long for N instructions on single-cycle (8ns clock period)?  $N \cdot 8ns = 8N ns$
- How much faster is pipelining for N=1000 ?


$$\frac{8 + 2N}{8N} \approx \frac{2000}{8000} \approx \frac{1}{4}$$
 
## Pipelining improves throughput at the cost of increased latency



# Some instructions do not require all five stages, can we skip stages?

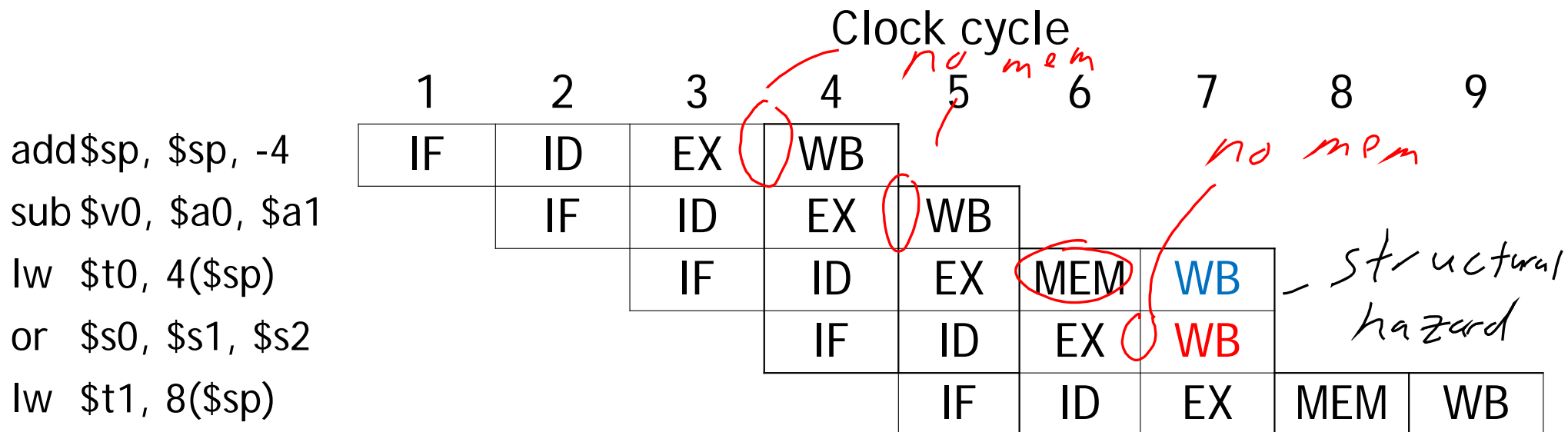- Example: R-type instructions only require 4 stages: IF, ID, EX, and WB
  - We don't need the MEM stage
- What happens if we try to pipeline loads with R-type instructions?




# Trying to use the single stage for multiple instructions creates a structural hazard

- Each functional unit can only be used **once** per instruction
- Each functional unit must be used at the **same** stage for all instructions:
  - Load uses Register File's Write Port during its **5th** stage
  - R-type uses Register File's Write Port during its **4th** stage

	Clock cycle								
	1	2	3	4	5	6	7	8	9
add\$sp, \$sp, -4	IF	ID	EX	WB					
sub \$v0, \$a0, \$a1		IF	ID	EX	WB				
lw \$t0, 4(\$sp)			IF	ID	EX	MEM	WB		
or \$s0, \$s1, \$s2				IF	ID	EX	WB		
lw \$t1, 8(\$sp)					IF	ID	EX	MEM	WB
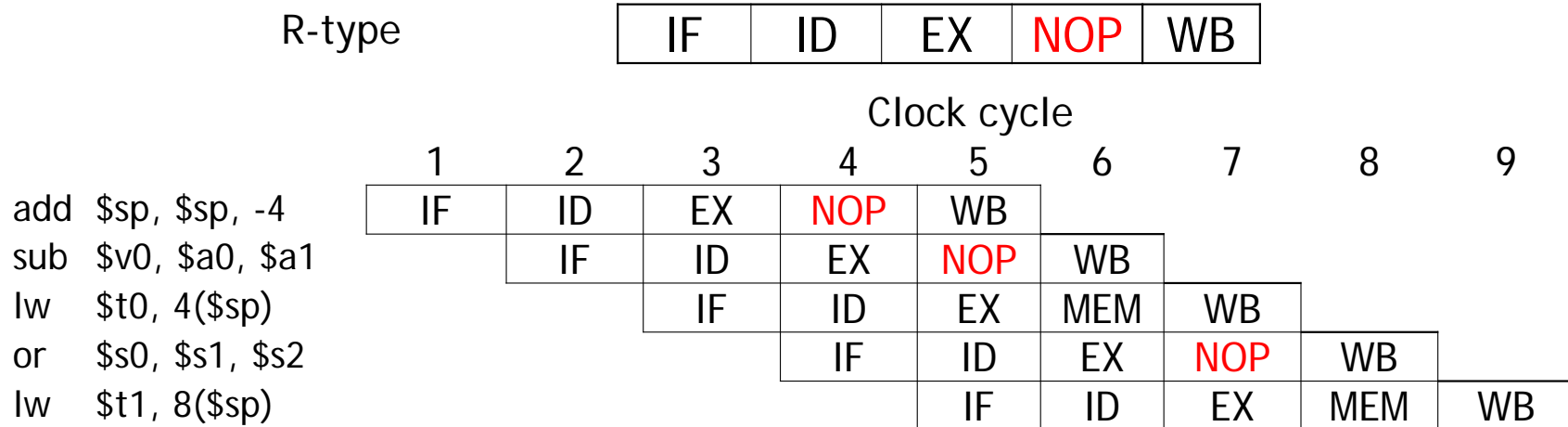
# Insert NOP stages to avoid structural hazards

- All instructions take 5 cycles with the same stages in the same order
  - Some stages will **do nothing** for some instructions




- Stores and Branches have **NOP** stages, too...

store	IF	ID	EX	MEM	NOP
branch	IF	ID	EX	NOP	NOP


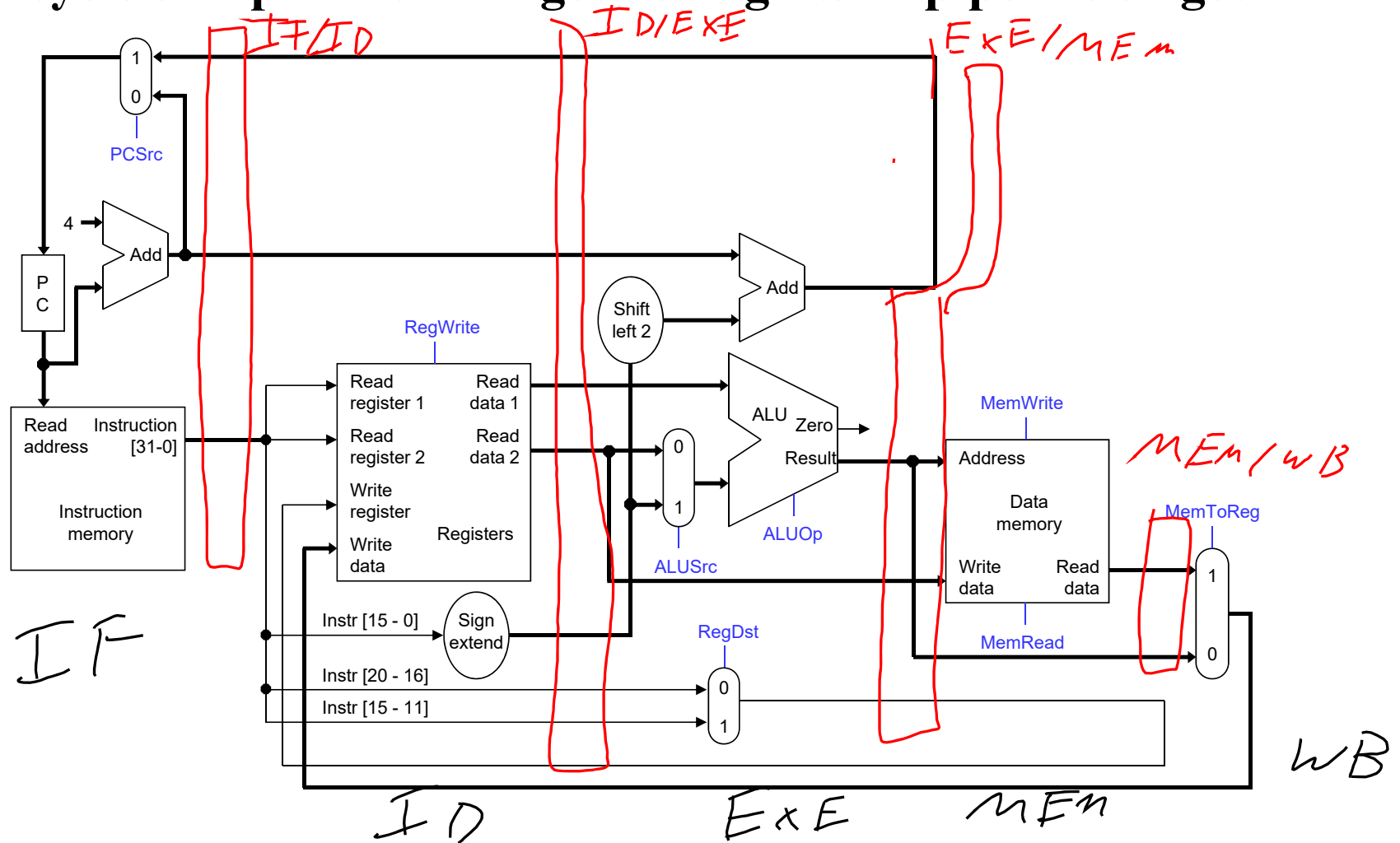
# Single-cycle datapath rearranged to align with pipeline stages




# Add pipeline registers in between stages

- There's a lot of information to save, however. We'll simplify our diagrams by drawing just one big **pipeline register** between each stage.
- The registers are named for the stages they connect.

IF/ID      ID/EX      EX/MEM      MEM/WB


- No register is needed after the WB stage, because after WB the instruction is done.
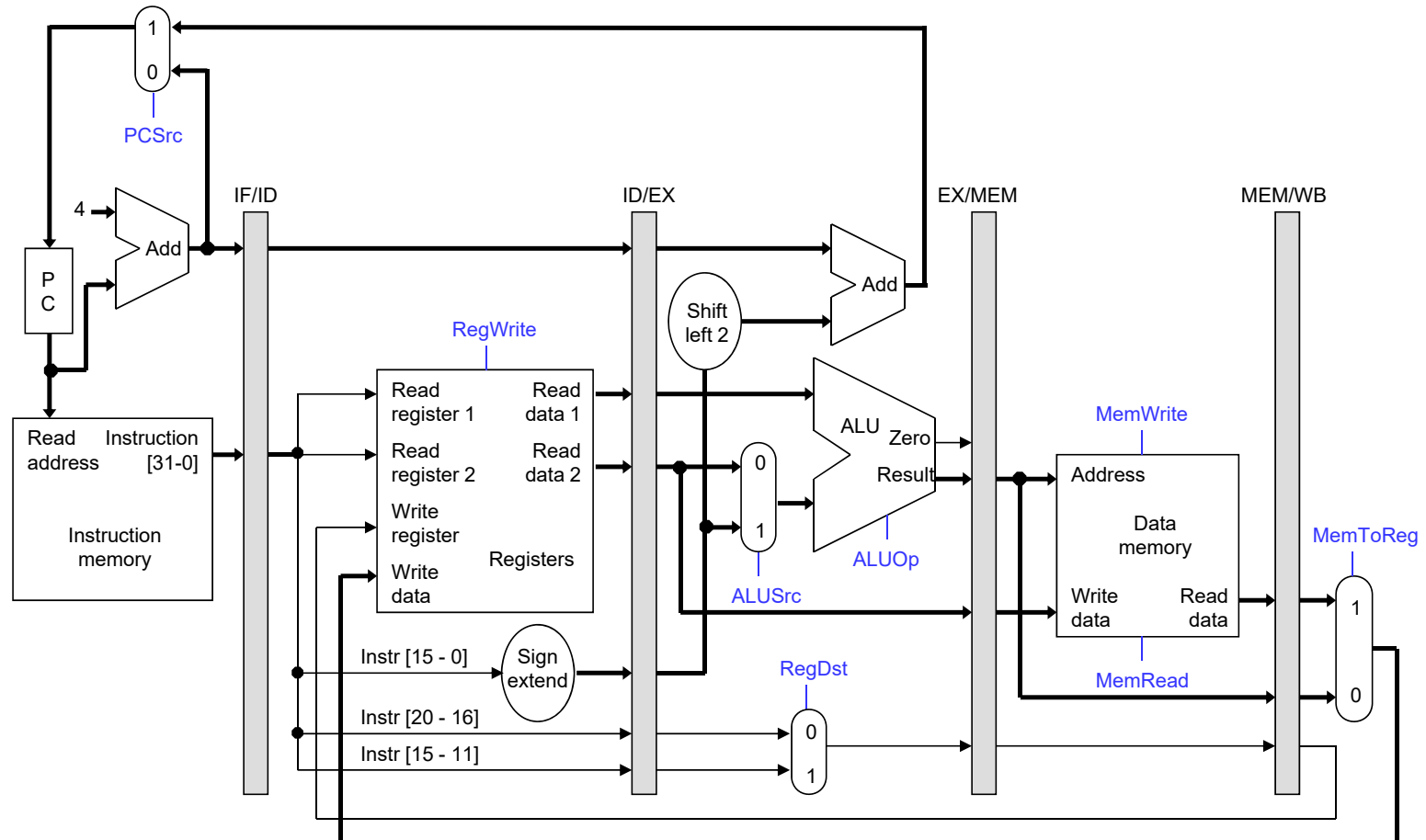
# Paths from register-read to register-write are now shorter




Data values required in later stages must be **propagated forward** through the pipeline registers.

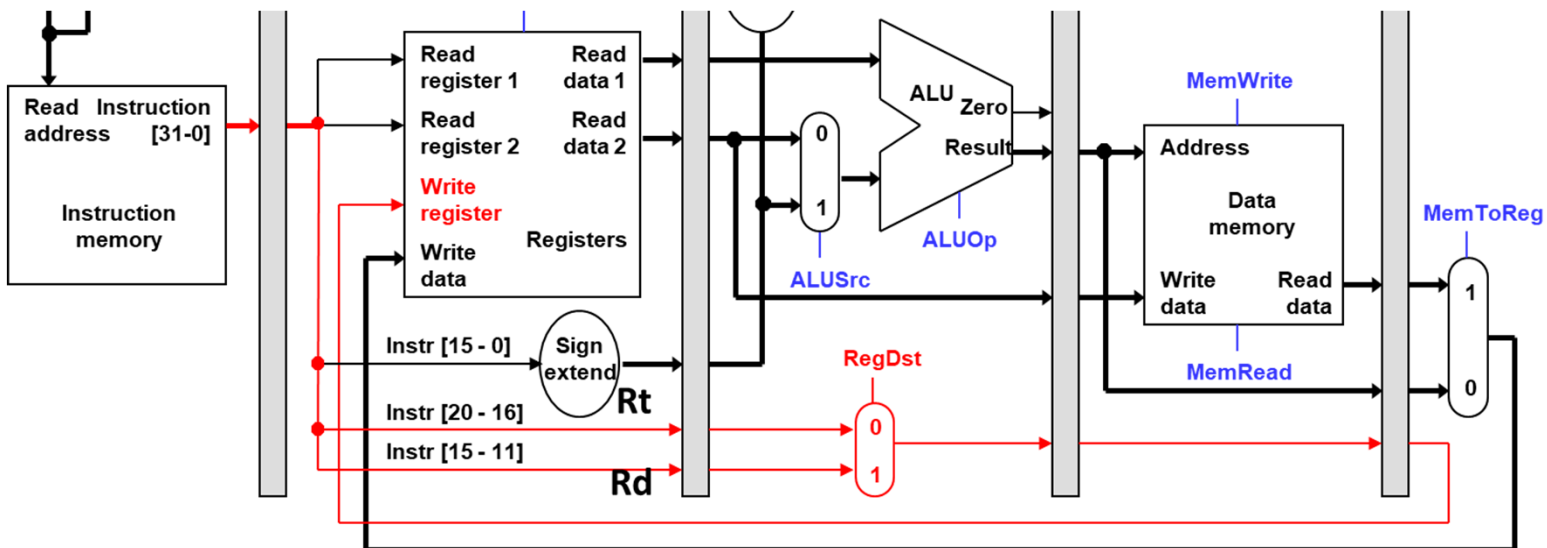
- Example
  - Destination register ( $rd$ ) is determined during the *first* stage (IF)
  - We store into the destination register during the *fifth* stage (WB)
  - $rd$  must be passed through all of the pipeline stages



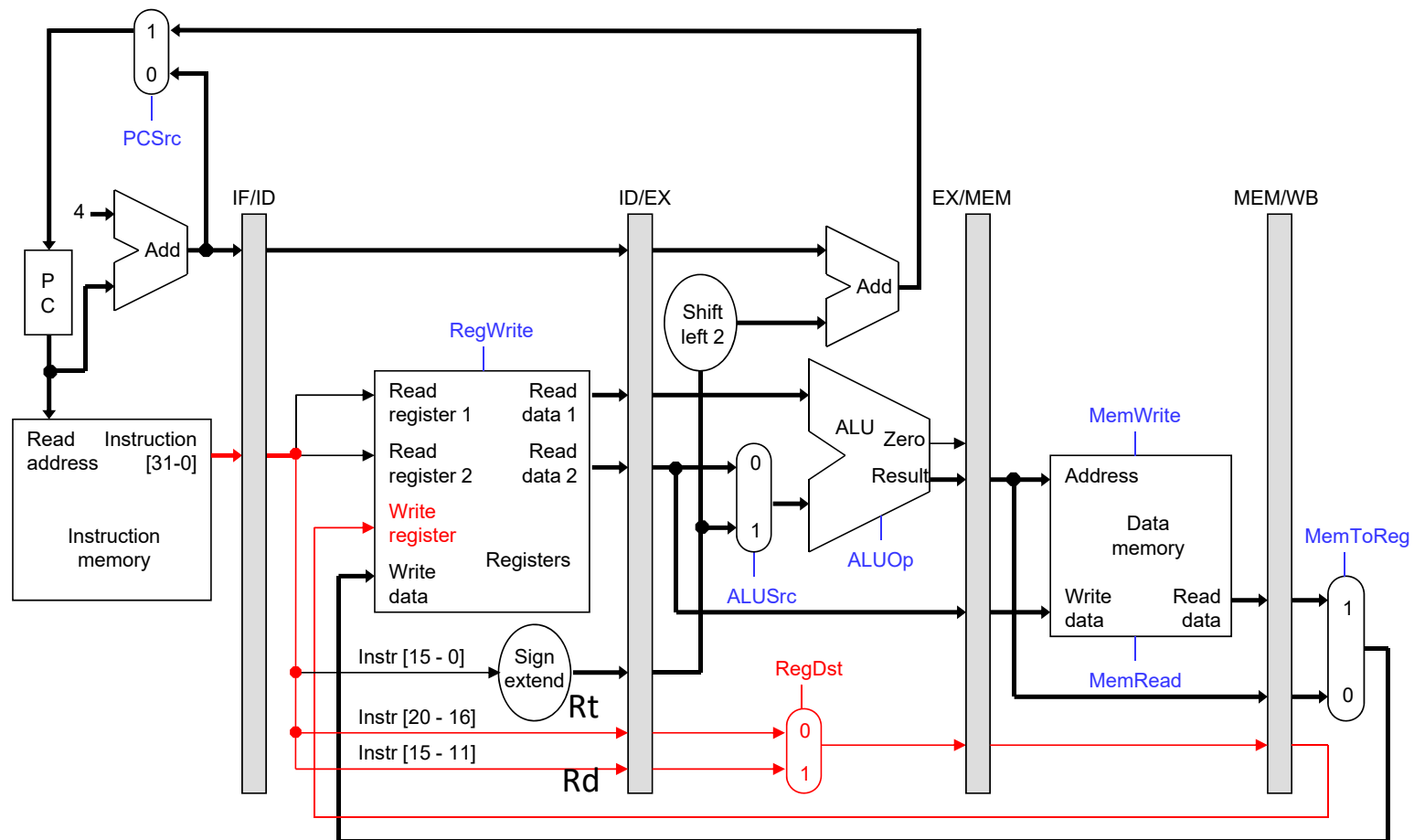**Note – We cannot keep values like destination register in the “instruction register”**



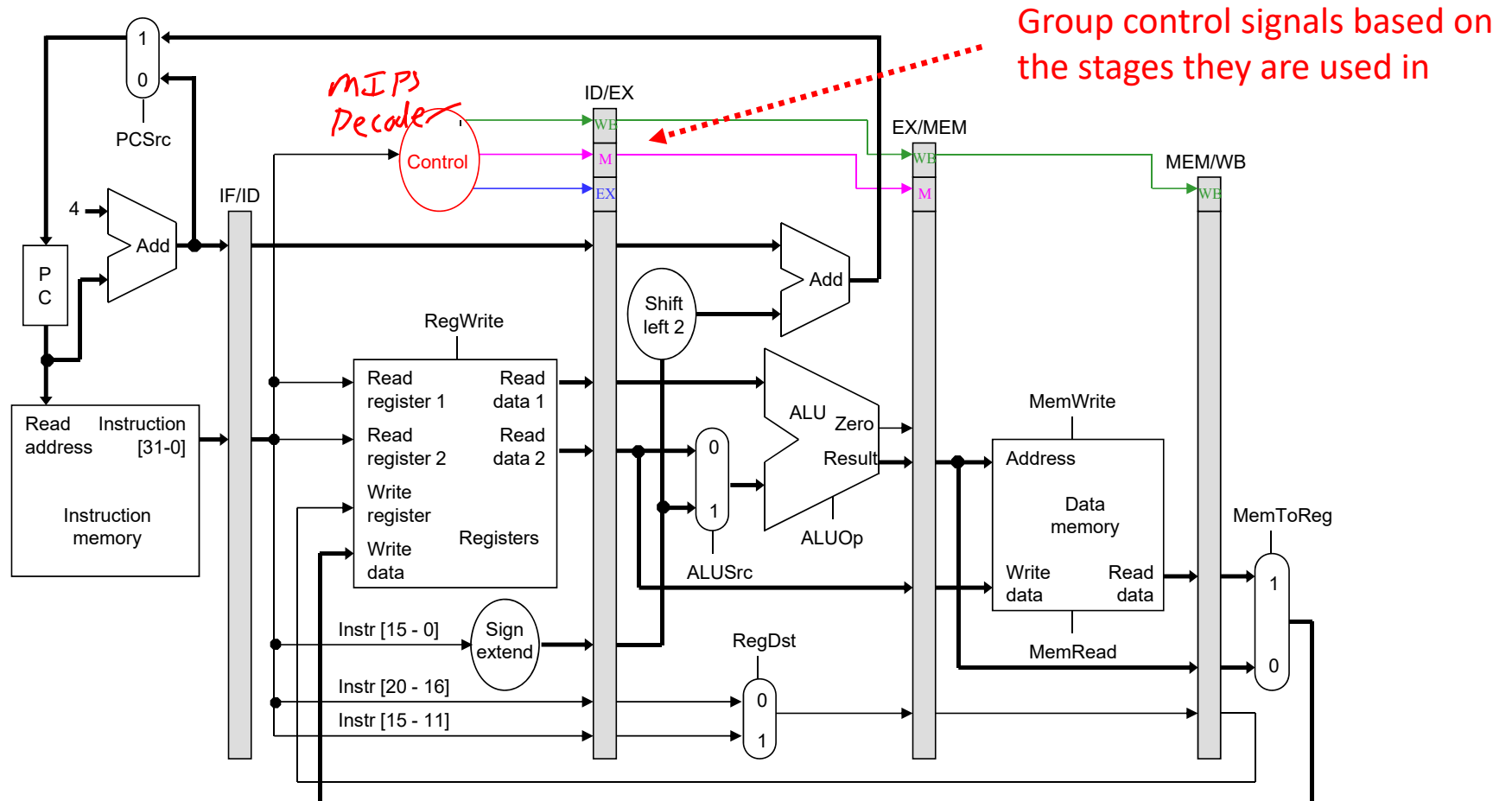
**Control signals are generated in the decode stage and are propagated across stages**



# Categorize control signals by the pipeline stage that uses them

Stage	Control signals needed			
EX	ALUSrc	ALUOp	RegDst	PCSrc
MEM	MemRead	MemWrite		
WB	RegWrite	MemToReg		

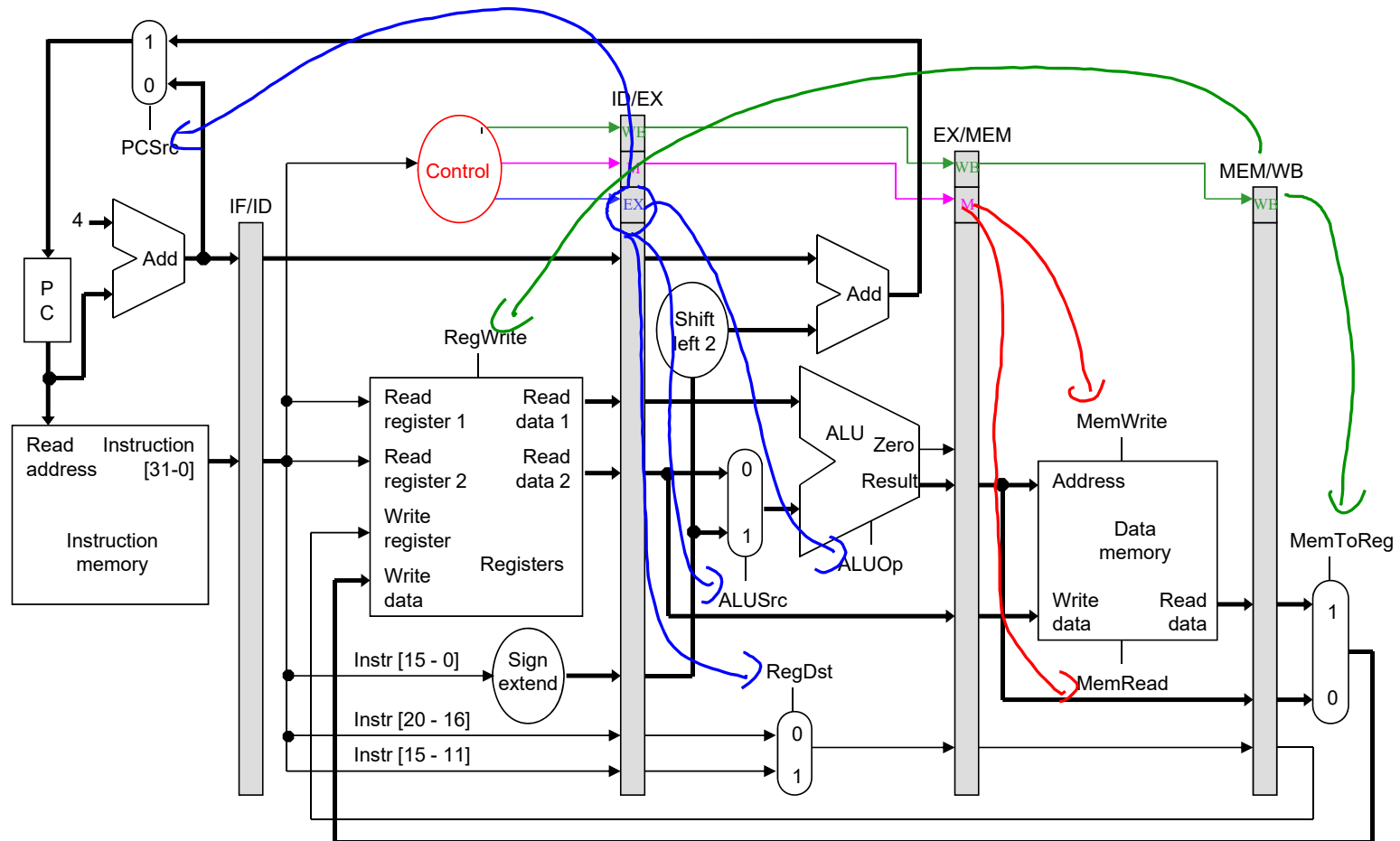**The pipeline registers and program counter update every clock cycle, so they do not have write enable controls**





# An example execution sequence

addresses in  
decimal



1000:	lw	\$8, 4(\$29)
1004:	sub	\$2, \$4, \$5
1008:	and	\$9, \$10, \$11
1012:	or	\$16, \$17, \$18
1016:	add	\$13, \$14, \$0


## ■ ASSUMPTIONS

- Each register contains its number plus 100. Example: R[8] == 108, R[29] == 129
- Every data memory location contains 99. Example: M[8] == 99, M[29] == 99


## ■ CONVENTIONS

- X indicates values that are not important, Example: Imm16 for R-type.
- Question marks ??? indicate values we do not know, usually resulting from instructions coming before and after the ones in our example.

## Cycle 1 (filling)

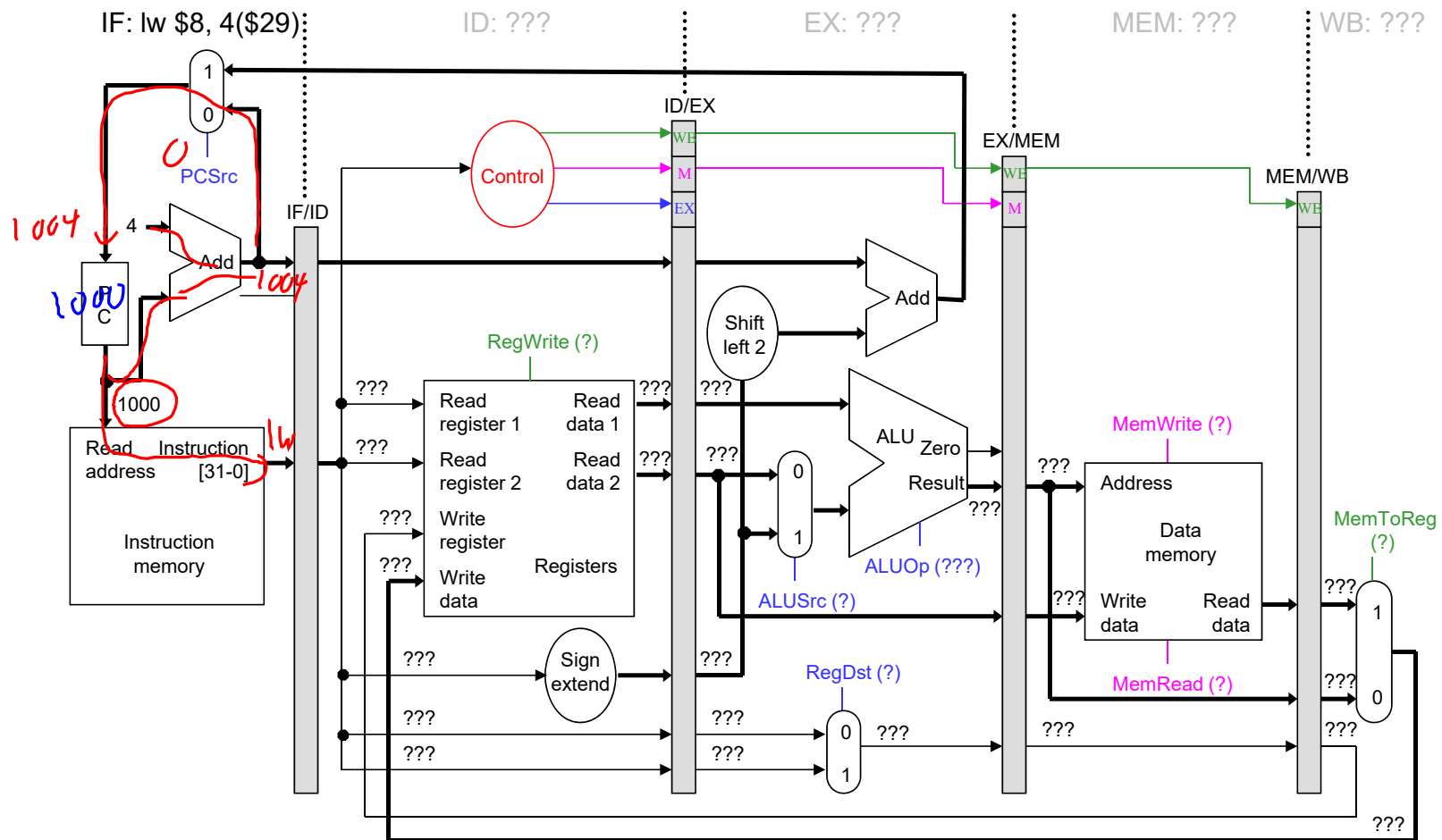

# Cycle 2

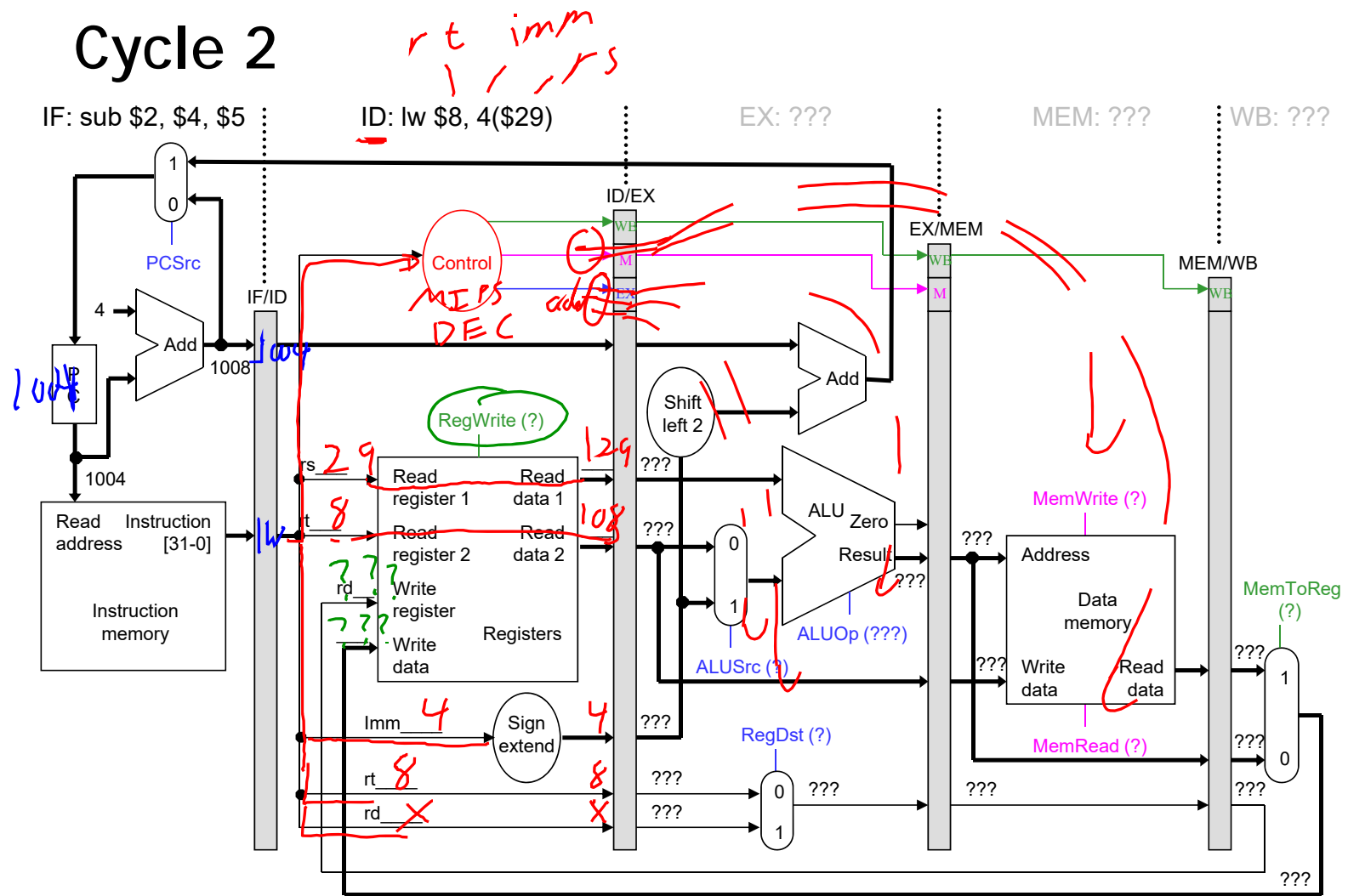

# Cycle 3


IF: and \$9, \$10, \$11

ID: sub \$2, \$4, \$5

EX: lw \$8, 4(\$29)


MEM: ???

WB: ???

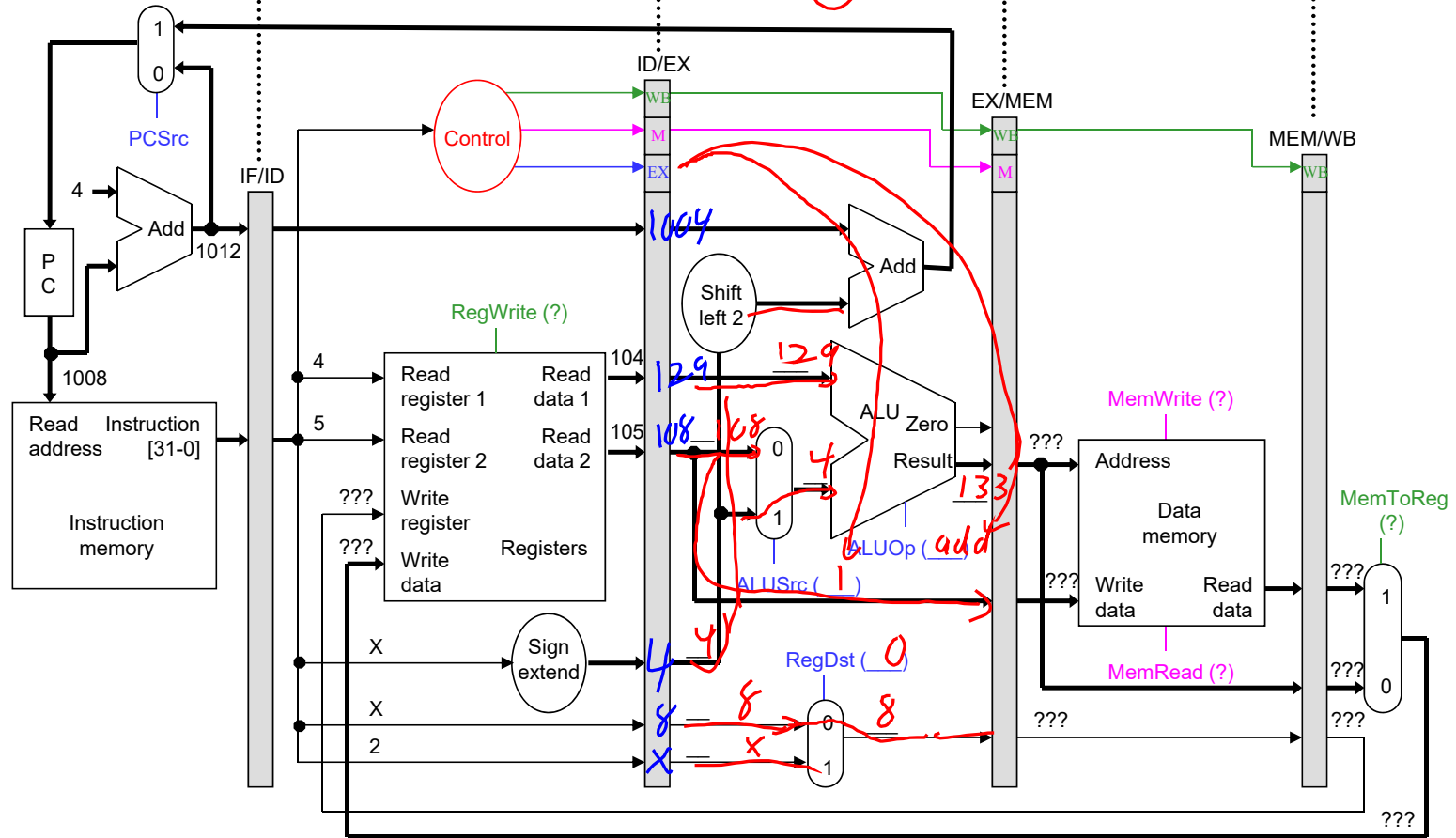

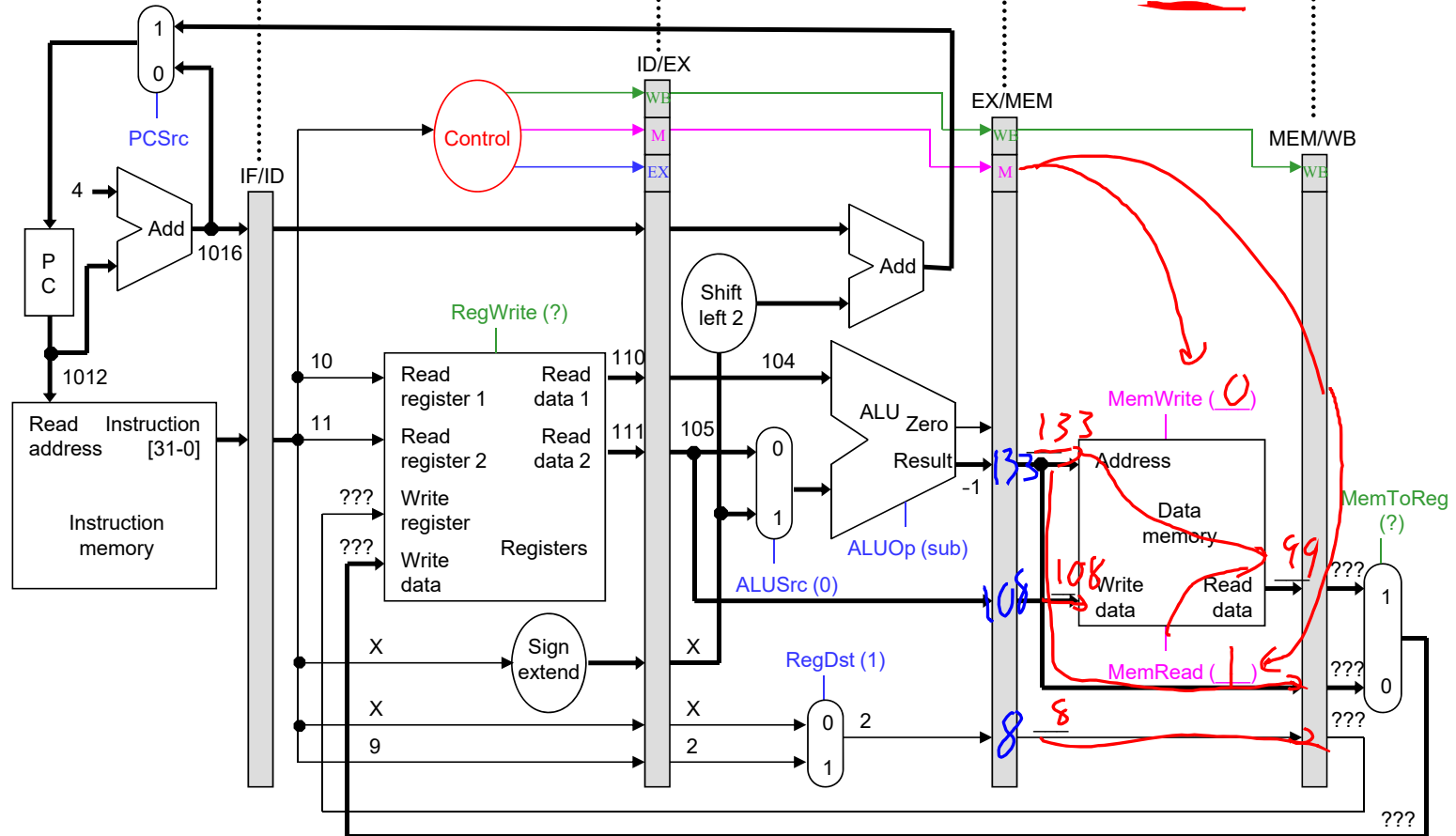
# Cycle 4

IF: or \$16, \$17, \$18 : ID: and \$9, \$10, \$11 : EX: sub \$2, \$4, \$5 : MEM: lw \$8, 4(\$29) : WB: ???



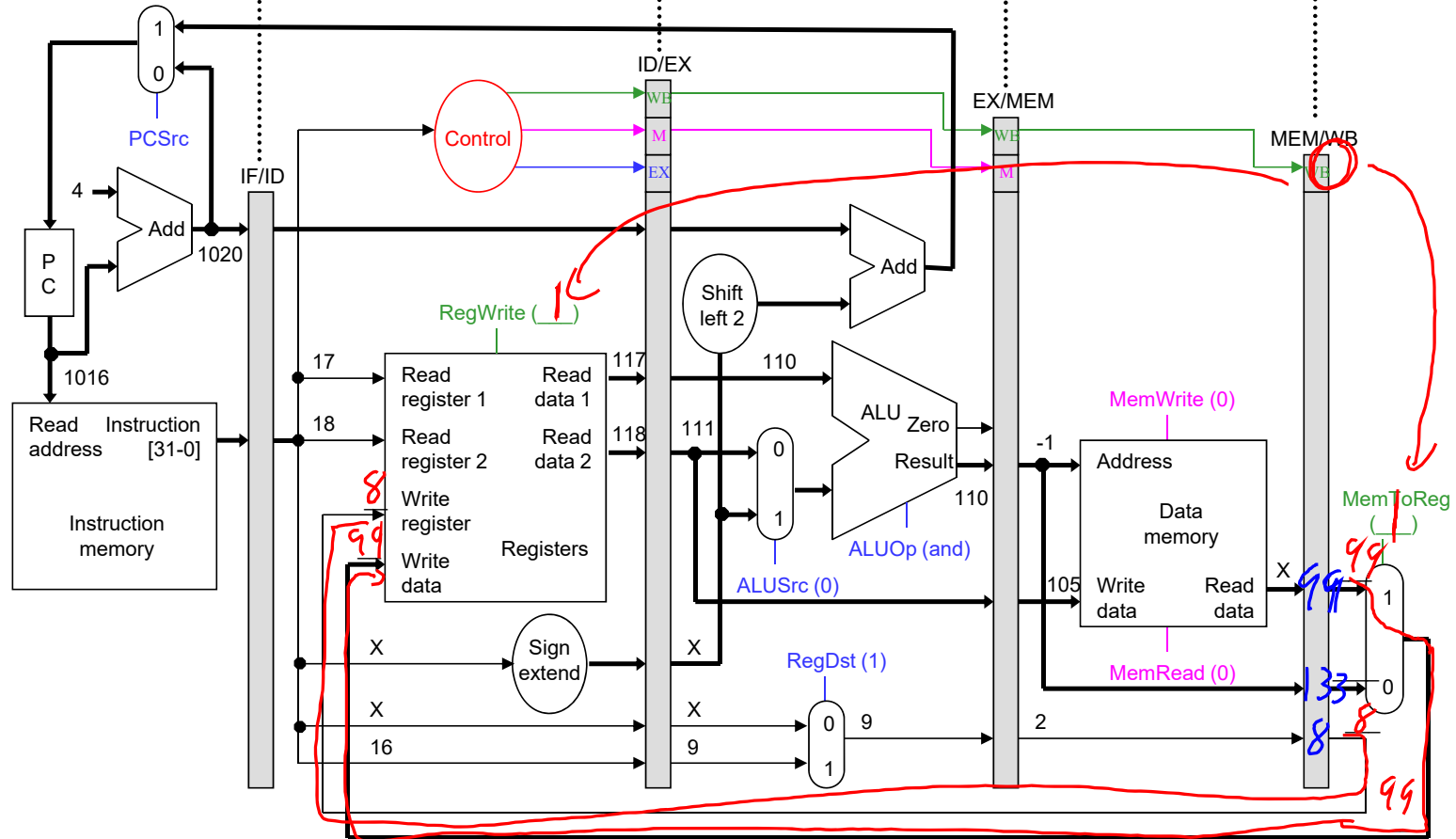
# Cycle 5 (full)


IF: add \$13, \$14, \$0      ID: or \$16, \$17, \$18      EX: and \$9, \$10, \$11      MEM: sub \$2, \$4, \$5      WB: lw \$8, 4(\$29)



# Cycle 6 (emptying)

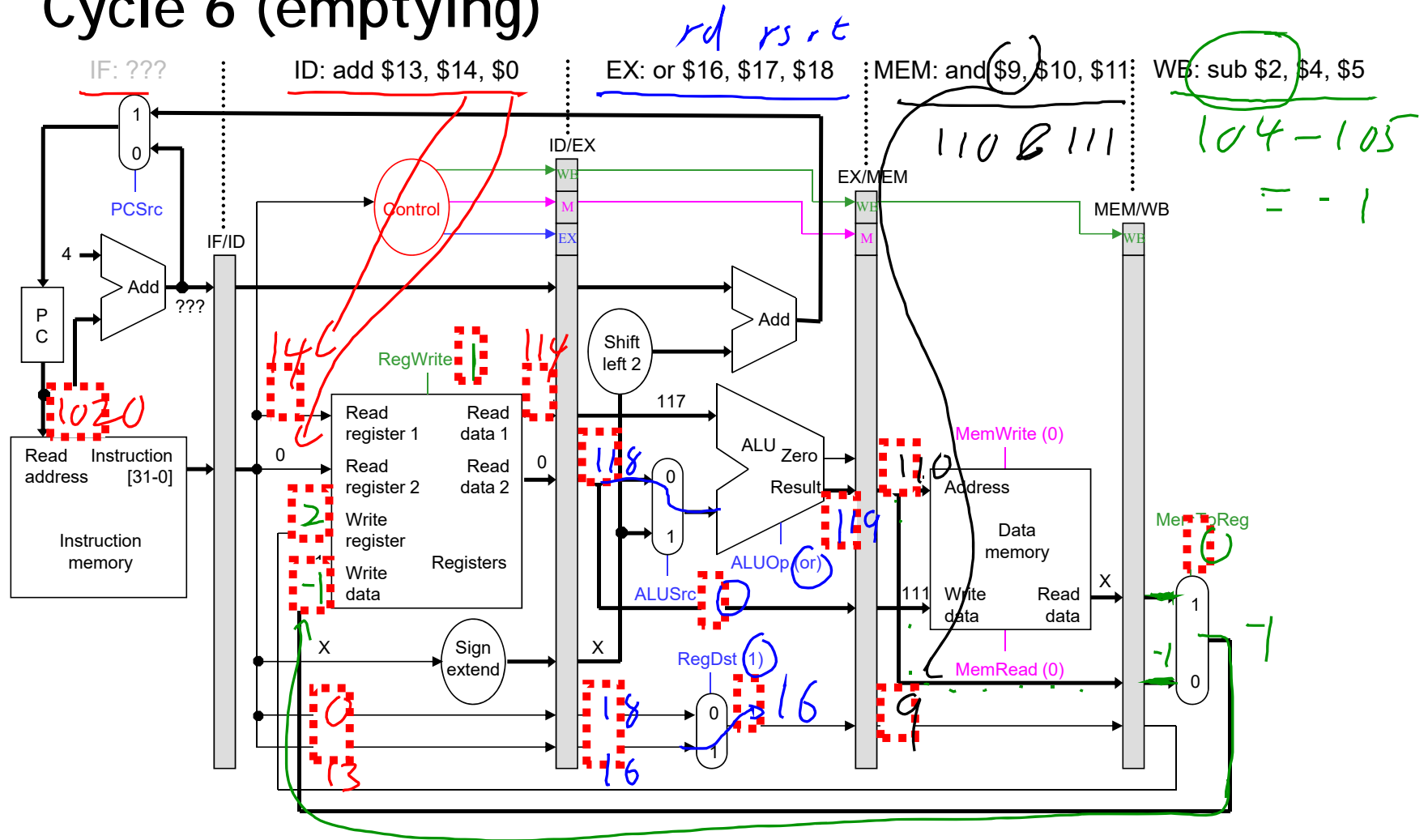


# Cycle 7

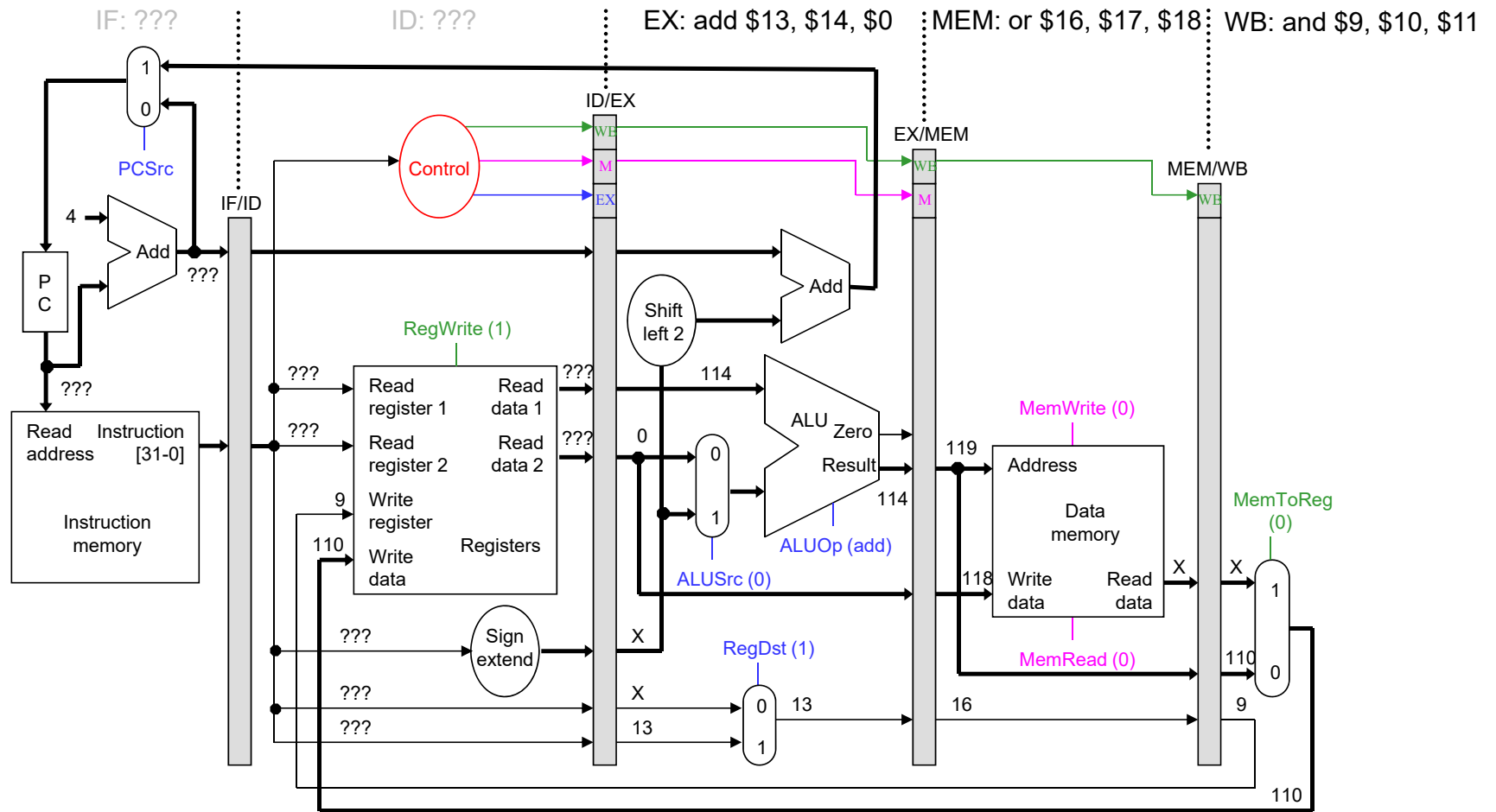




# Cycle 8

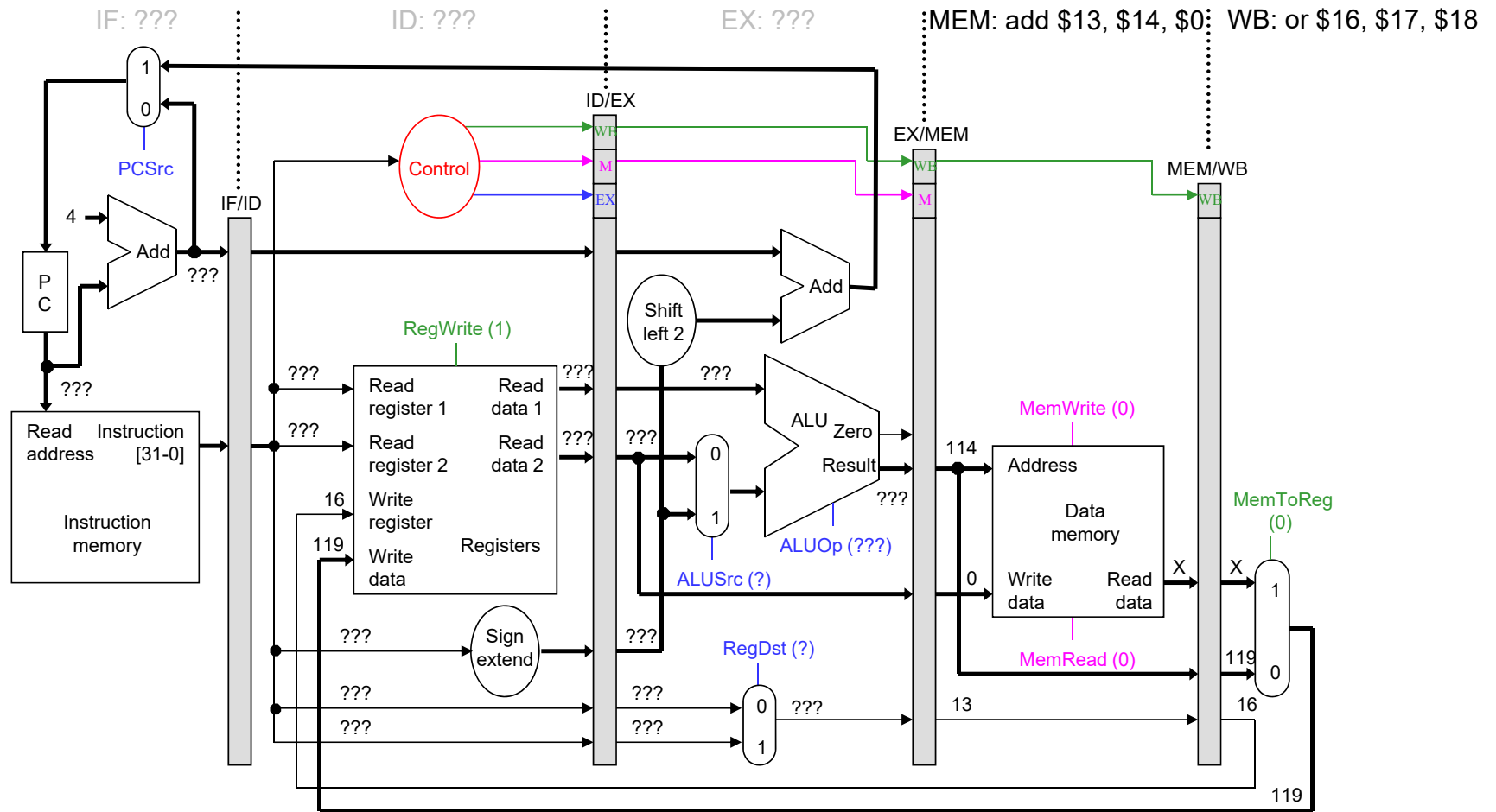

# Cycle 9

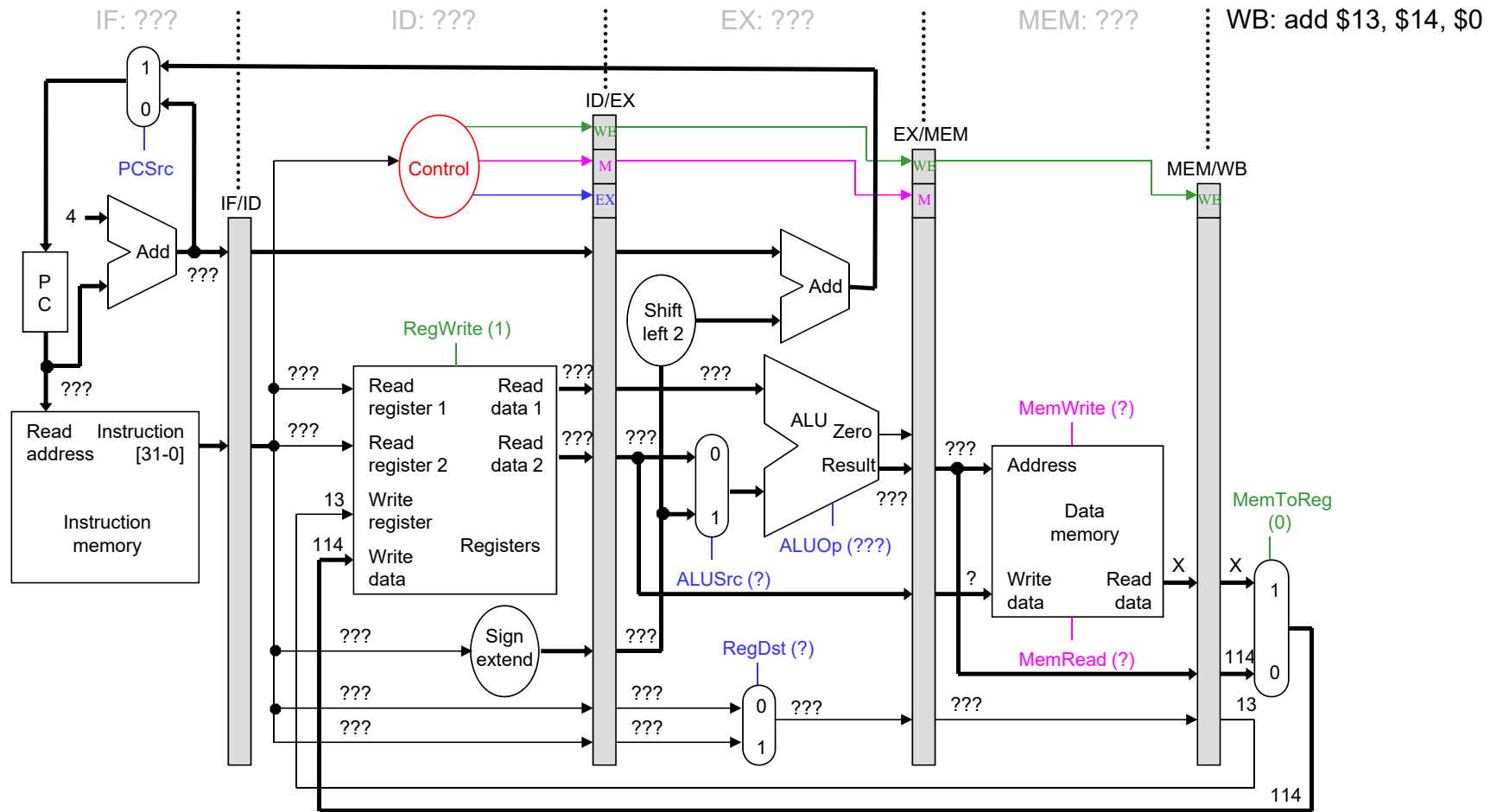

# Things to notice from the last nine slides


	Clock cycle								
	1	2	3	4	5	6	7	8	9
add \$sp, \$sp, -4	IF	ID	EX	NOP	WB				
sub \$v0, \$a0, \$a1		IF	ID	EX	NOP	WB			
lw \$t0, 4(\$sp)			IF	ID	EX	MEM	WB		
or \$s0, \$s1, \$s2				IF	ID	EX	NOP	WB	
lw \$t1, 8(\$sp)					IF	ID	EX	MEM	WB

- Instruction executions overlap
- Each functional unit is used by a *different* instruction in each cycle.
- In clock cycle 5, all of the hardware units are used (the pipeline is full). This is the ideal situation, and what makes pipelined processors so fast
- Similar example in the book available at the end of Section 6.3.

# **MIPs ISA makes pipelining “easy”**

- Instruction formats are the same length and uniform
- Addressing modes are simple
- Each instruction takes only one cycle

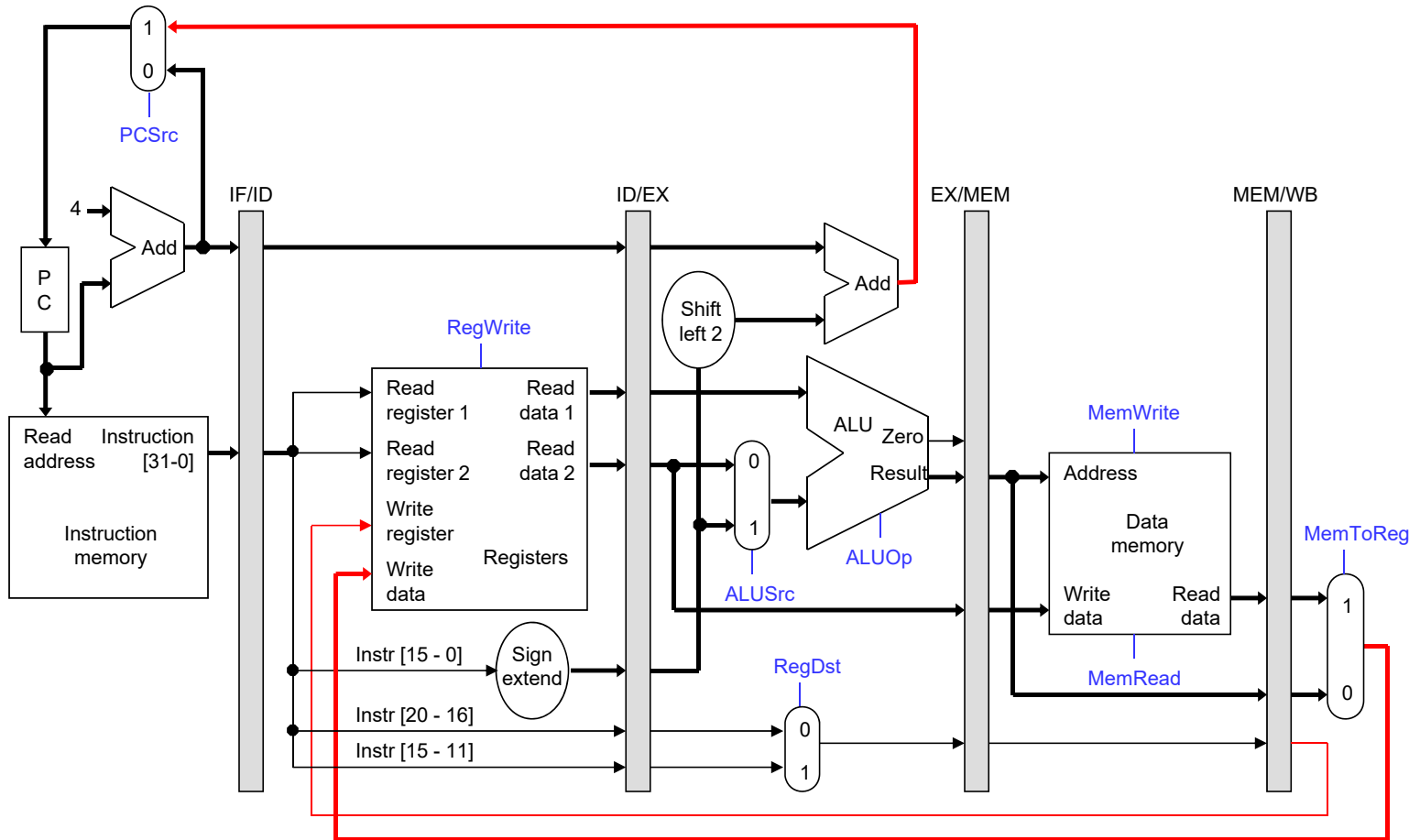
**Note how everything goes left to right, except ...**



Next time: We  
will discuss Data  
Hazards



# Cycle 6 (emptying)

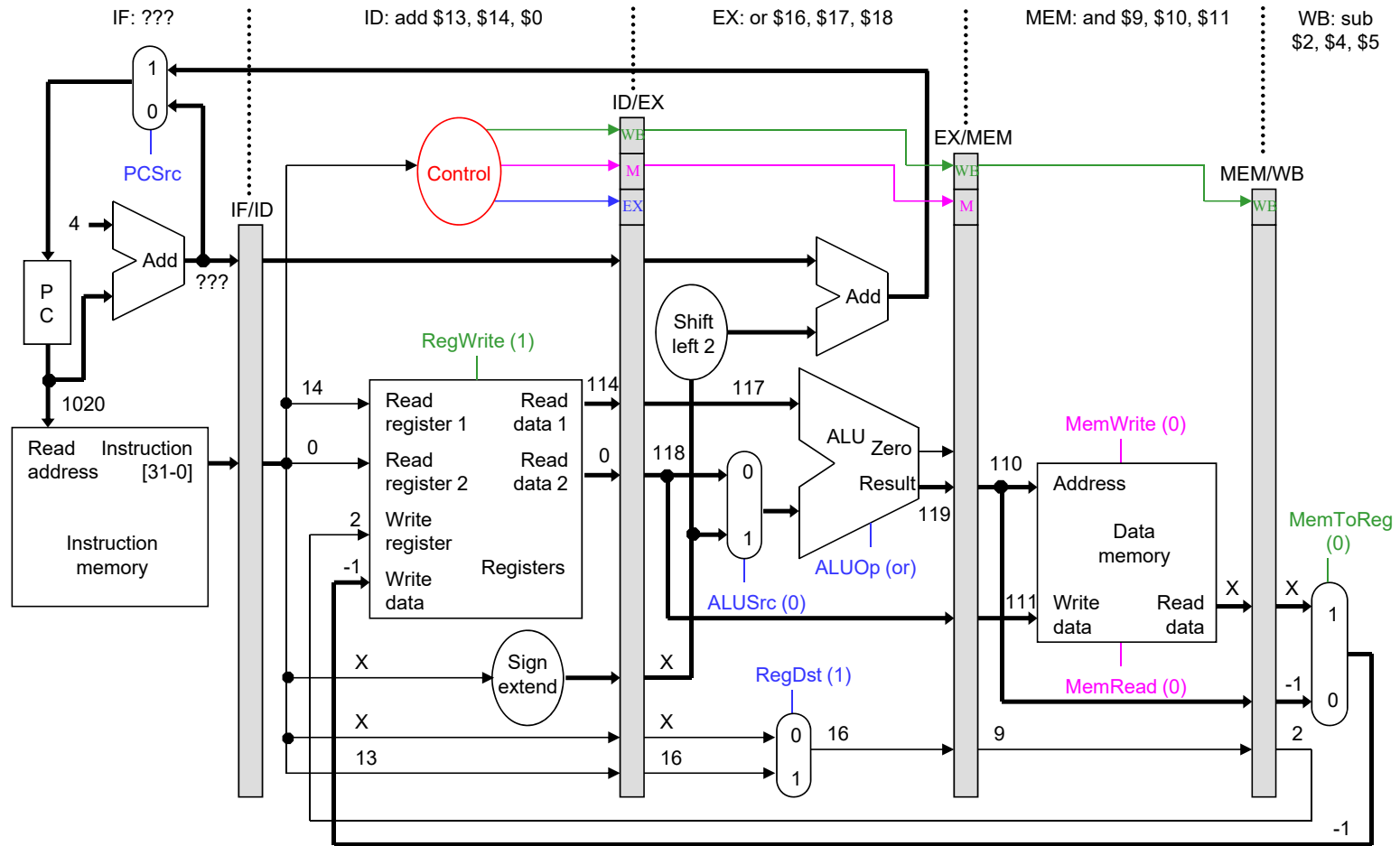

October 30, 2017

Pipelined datapath and control

38